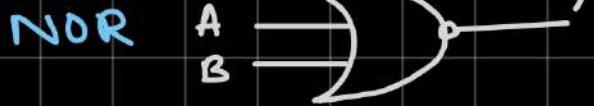


UNIT - 1

BASIC FUNCTION/GATES



A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0



A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

BOOLEAN FUNCTION: algebraic expression consists of binary variables and logic operations

$$\text{Ex: } F = x + y'z$$

Number of rows in truth table = 2^n

Binary number - counting from 0 through $2^n - 1$


Q. $F = x + y'z$. Write the TT & gate implementation



$$Q. \quad F = x'y'z + x'yz + xy'$$

$$F = x'y'z + x'yz + xy' = x'z + xy'$$

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

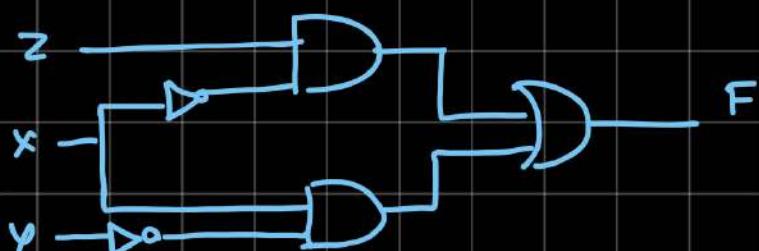

BOOLEAN IDENTITIES/LAWS

principle of duality: $+ \leftrightarrow \cdot$ then $0 \leftrightarrow 1$

	LAW	DUAL LAW
COMMUTATIVE	$a \cdot b = b \cdot a$	$a + b = b + a$
ASSOCIATIVE	$(a \cdot b) \cdot c = a \cdot (b \cdot c)$	$(a+b)+c = a+(b+c)$
DISTRIBUTIVE	$a \cdot (b+c) = a \cdot b + a \cdot c$	$a+(b \cdot c) = (a+b) \cdot (a+c)$
DEMORGAN	$(a+b)' = a' \cdot b'$	$(a \cdot b)' = a' + b'$
IDEMPOTENCY	$a \cdot a = a$	$a + a = a$
IDENTITY	$a \cdot 1 = a$	$a + 0 = a$
BOUNDEDNESS	$a \cdot 0 = 0$	$a + 1 = 1$
COMPLEMENT	$a \cdot \bar{a} = 0$	$a + \bar{a} = 1$
ABSORPTION	$a + a \cdot b = a$	$a \cdot (a+b) = a$
INVOLUTION	$a = a$	$a = a$
USEFUL IDENTITY	$a + \bar{a} \cdot b = a + b$	$a \cdot (\bar{a} + b) = a \cdot b$

Q. Simplify the following Boolean expression

1. $x(x'+y) = x \cdot x' + xy = xy$
2. $x+x'y = (x+x')(x+y) = 1(x+y) = x+y$
3. $(x+y)(x+y') = x + xy' + xy + y \cdot y' = x(1+y'+y) = x$
4. $xy + x'z + yz = xy + x'z + yz(x+x') = xy + xz + xyz + x'yz$
 $= xy(1+z) + x'z(1+y) = xy + x'z$
5. $(x+y)(x'+z)(y+z) = (x+y) \cdot (x'+z)$
(Duality of the previous question)

Q. Find complement & duality

1. $F_1 = (x'yz' + x'y'z)$ Duality: $(x'+y+z') \cdot (x'+y'+z)$
Complement: $F_1' = (x+y'+z)(x+y+z')$
2. $F_2 = x(y'z' + yz)$ Duality: $x + (y'+z') \cdot (y+z)$
Complement: $F_2' = x' + (y+z)(y'+z')$

CANONICAL / STANDARD FORMS

			MINTERMS		MAXTERMS	
X	Y	Z	Term	Designation	Term	Designation
0	0	0	$x'y'z'$	m_0	$x+y+z$	M_0
0	0	1	$x'y'z$	m_1	$x+y+z'$	M_1
0	1	0	$x'yz'$	m_2	$x+y'+z$	M_2
0	1	1	$x'yz$	m_3	$x+y'+z'$	M_3
1	0	0	$xy'z'$	m_4	$x'+y+z$	M_4
1	0	1	$xy'z$	m_5	$x'+y+z'$	M_5
1	1	0	xyz'	m_6	$x'+y'+z$	M_6
1	1	1	xyz	m_7	$x'+y'+z'$	M_7

$2^n \rightarrow$ distinct min/max terms (SOP) (Σ)

No. of function = 2^{2^n}
as a product of max/min terms

(POS) (Π)

Max $\rightarrow 0 = a$
Min $\rightarrow 0 = a'$

Q. Find minterms for $F = A + B'C$

$$F(A, B, C) = \Sigma(1, 4, 5, 6, 7)$$

Q. Express $F = xy + x'z$ as product of maxterms

$$F(x, y, z) = \Pi(0, 2, 4, 5)$$

Q. Find min & maxterms for

① 00011011

$$\text{SOP} = \Sigma(3, 4, 6, 7)$$

$$\text{POS} = \Pi(0, 1, 2, 5)$$

② 01011010

$$\text{SOP} = \Sigma(1, 3, 4, 6)$$

$$\text{POS} = \Pi(0, 2, 5, 7)$$

GATE MINIMIZATION [K-MAPS]

K-map → Karnaugh map


IMPLICANT → composed of squares containing 1's
 No. of squares in 2^n
 double the area → one less literal

PRIME IMPlicant → Largest no. of squares obeying rules


ESSENTIAL PRIME IMPlicant → containing square in no other prime implicant

→ include all required prime implicants

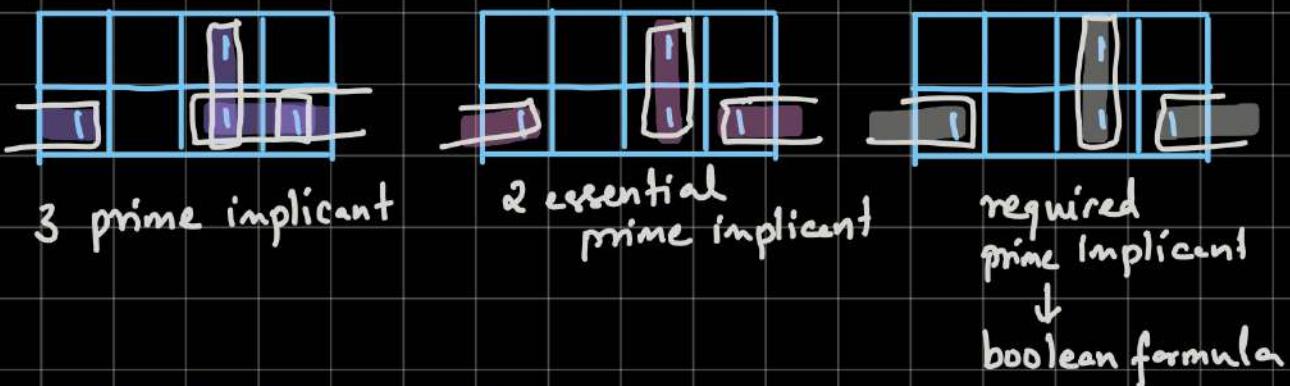→ Convert required implicants to Boolean formula.



TWO VARIABLE K-MAP

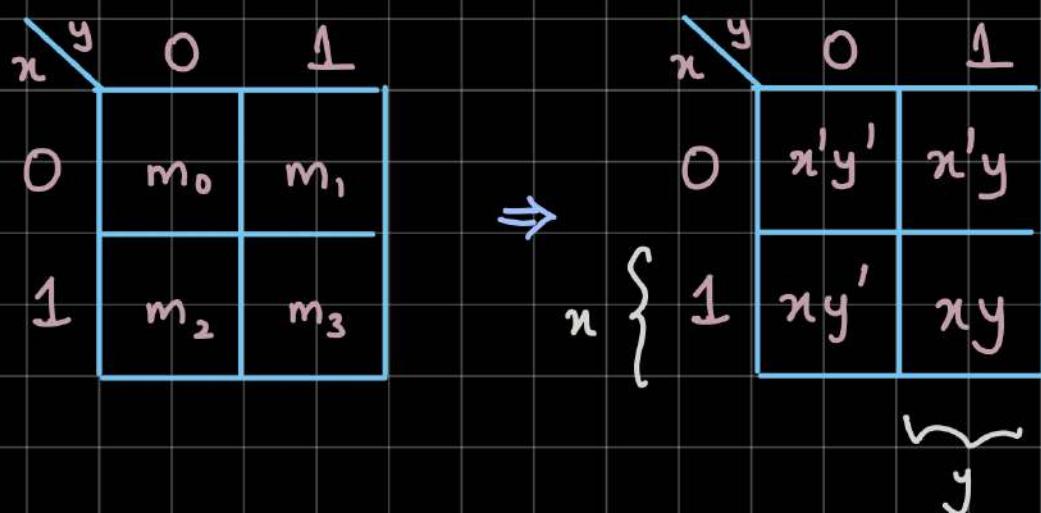

THREE VARIABLE K-MAP

	$x'y'z$	00	01	$\overbrace{11}^y$	10
0	m_0	m_1	m_3	m_2	
1	m_4	m_5	m_7	m_6	
n				\overbrace{z}	


	$x'y'z'$	00	01	$\overbrace{11}^y$	10
0	$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$	
1	$xy'z'$	$xy'z$	xyz	xyz'	
n				\overbrace{z}	

FOUR VARIABLE K-MAP


	$wx'y'z$	00	01	$\overbrace{11}^y$	10
00	m_0	m_1	m_3	m_2	
01	m_4	m_5	m_7	m_6	
11	m_{12}	m_{13}	m_{15}	m_{14}	
10	m_8	m_9	m_{11}	m_{10}	
n				\overbrace{z}	

	$w'x'y'z$	00	01	$\overbrace{11}^y$	10
00	$w'x'y'z$	$w'x'y'z$	$w'x'yz$	$w'x'yz'$	
01	$w'xy'z$	$w'xy'z$	$w'xyz$	$w'xyz'$	
11	$wxy'z'$	$wxy'z$	$wxyz$	$wxyz'$	
10	$wx'y'z'$	$wx'y'z$	$wx'yz$	$wx'yz'$	
w				\overbrace{z}	

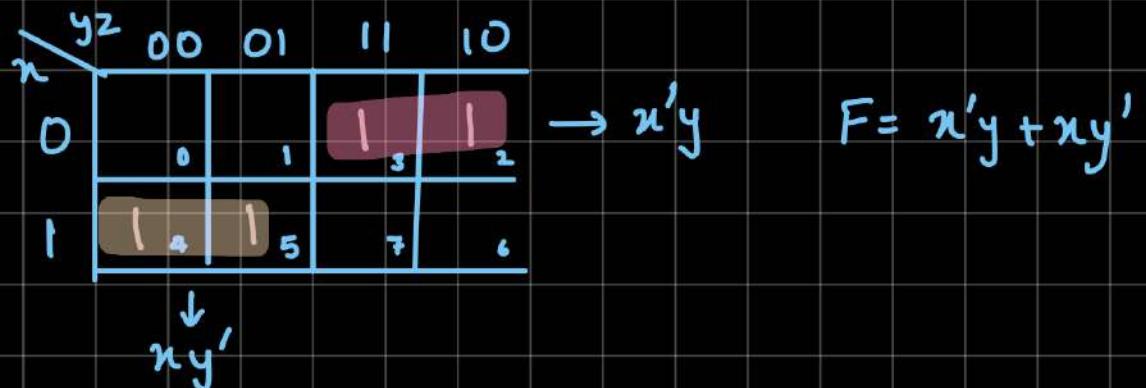
① Simplify the Boolean fn $F(x,y,z) = \Sigma(2,3,4,5)$




② $F(x,y,z) = \Sigma(3,4,6,7)$

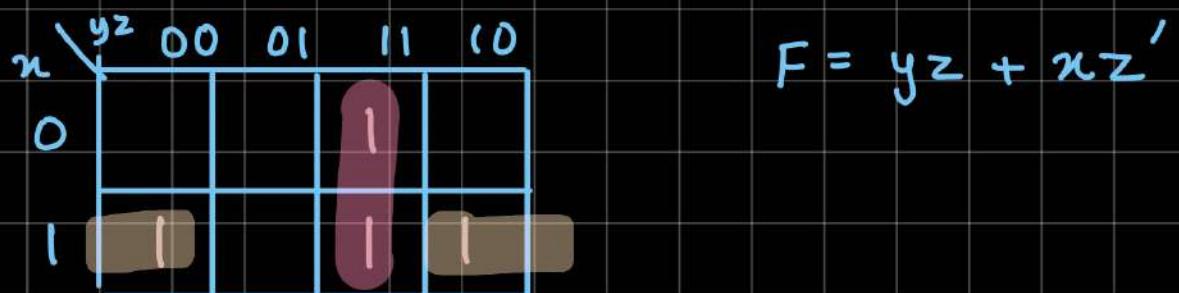


③ $F(x,y,z) = \Sigma(0,2,4,5,6)$

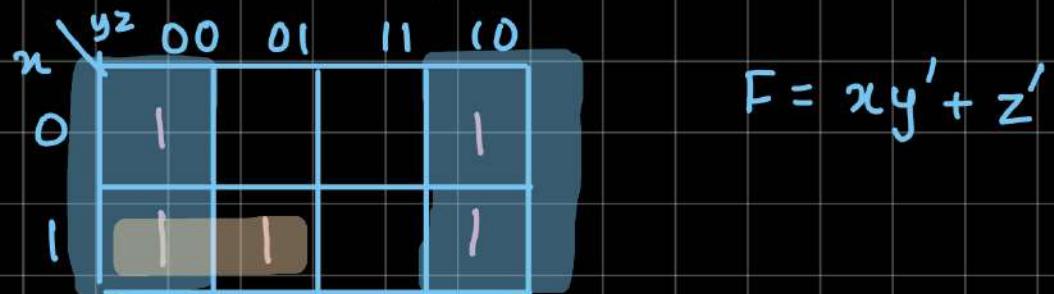

④ $F(x,y,z) = \Sigma(0,1,6,7)$

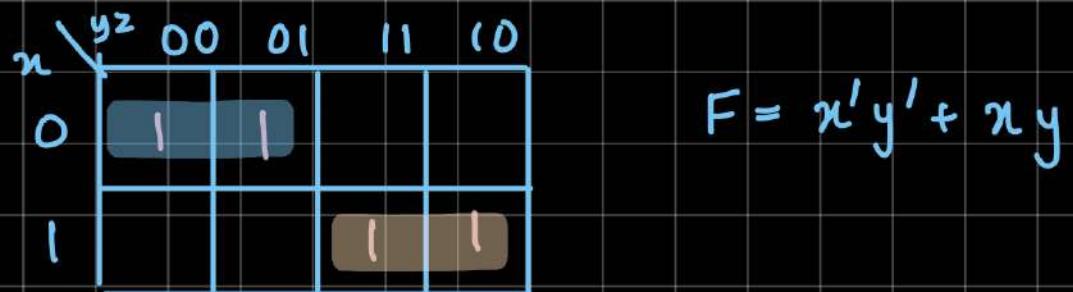

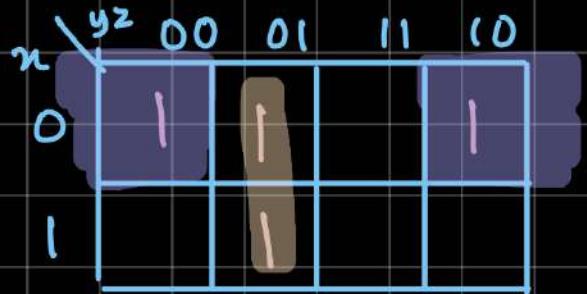
$$\textcircled{5} \quad F(x,y,z) = \sum(0,1,2,5)$$




$$F = x'z' + y'z$$
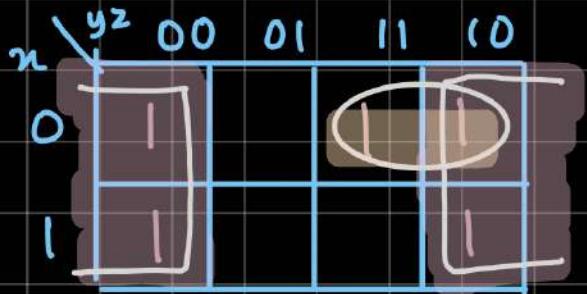
$$\textcircled{6} \quad F(x,y,z) = \sum(0,2,3,4,6)$$



$$F = z' + x'y$$
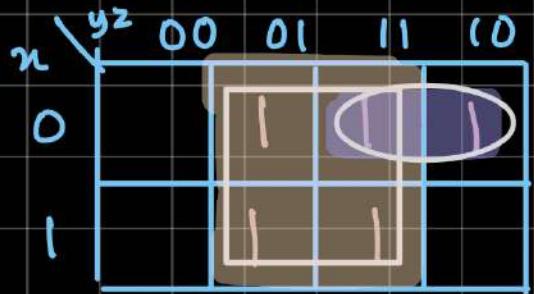
$$\textcircled{7} \quad F(x,y,z) = \sum(1,2,3,5,7)$$




$$F = z + x'y$$

$$\textcircled{8} \quad F(A,B,C) = A'C + AB'C + BC + A'B$$

(a) Express as a sum of minterms

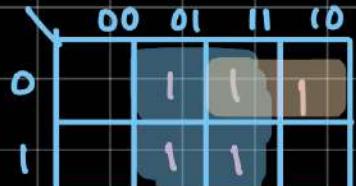(b) Find the minimal SOP

$$\begin{aligned}
 F(A,B,C) &= A'C(B+B') + AB'C + (A+A')BC + A'B(C+C') \\
 &= A'BC + A'B'C + AB'C + ABC + A'BC \\
 &\quad + A'BC + A'BC' \\
 &= A'BC + A'B'C + AB'C + ABC + A'BC' \\
 &= m_3 + m_1 + m_5 + m_7 + m_2 = \sum(1,2,3,5,7)
 \end{aligned}$$



$$F = C + \bar{A}B$$

$$\textcircled{9} \quad F(A, B, C) = \sum(1, 2, 3, 5, 6, 7)$$

A	B	C	00	01	11	10
0	0	0				
1	1	0				
			1	1	1	1

$$F = C + B$$

$$\textcircled{10} \quad F(A, B, C) = \sum(0, 1, 2, 4, 5, 6)$$

A	B	C	00	01	11	10
0	0	0				
1	1	0				
			1	1	1	1

$$F = B' + C'$$

$$\textcircled{11} \quad F(A, B, C) = \sum(0, 2, 3, 4, 6, 7)$$

A	B	C	00	01	11	10
0	0	0				
1	1	0				
			1	1	1	1


$$F = C' + B$$

$$\textcircled{12} \quad F(A, B, C) = \sum(0, 3, 5)$$

A	B	C	00	01	11	10
0	0	0				
1	1	0				
			1	1		


$$F = \bar{A}\bar{B}\bar{C} + A\bar{B}C + \bar{A}BC$$
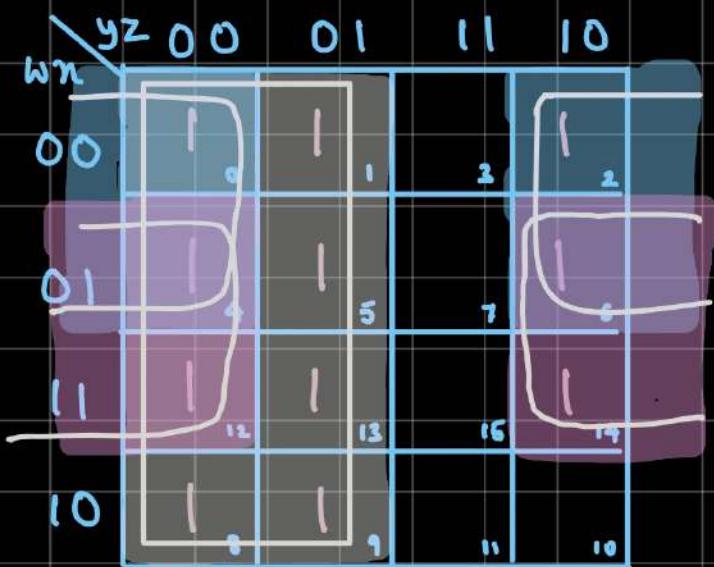
$$⑬ F(w, x, y, z) = \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$$




$$F = y' + w'z' + xz'$$
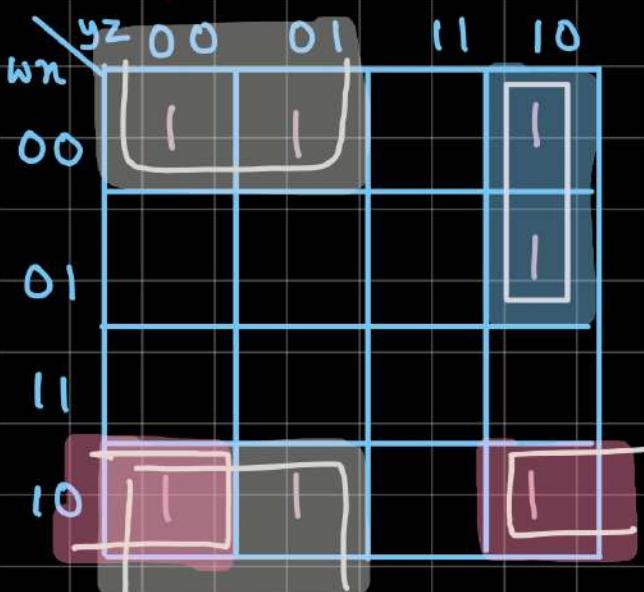
$$⑭ F(w, x, y, z) = \Sigma(0, 1, 2, 6, 8, 9, 10)$$




$$F = x'y' + w'yz' + wu'z'$$
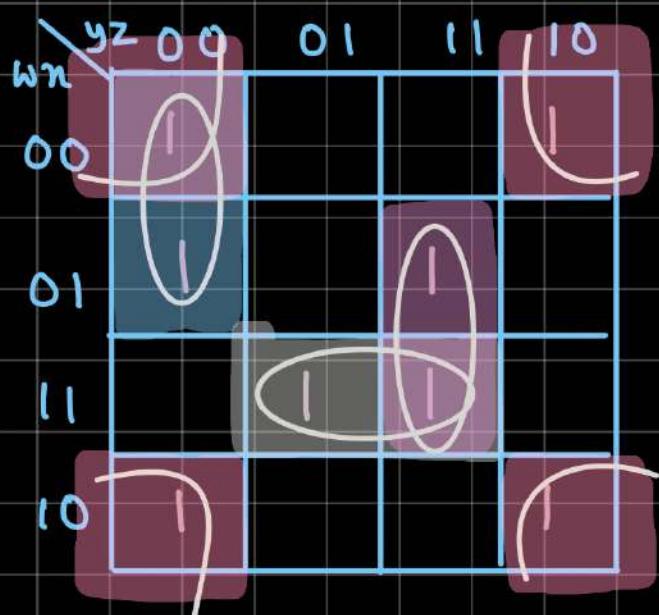
$$⑮ F(w, u, y, z) = \Sigma(0, 2, 5, 7, 8, 10, 13, 15)$$




$$F = w'y'z' + wu'z + xyz + u'z'$$
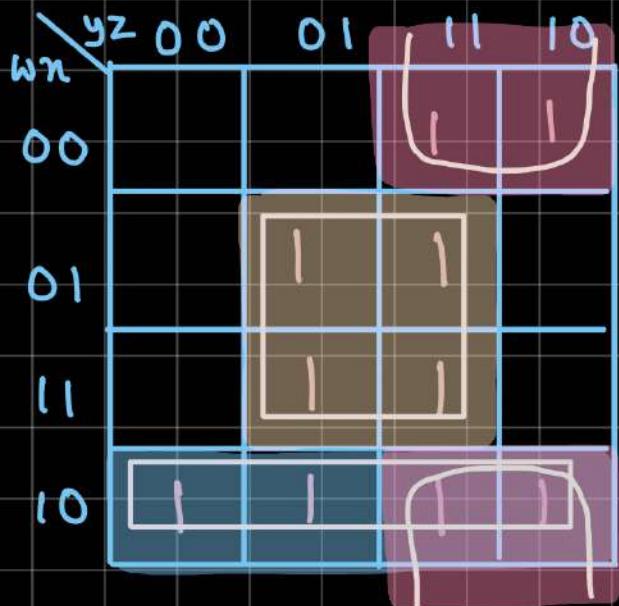
$$⑯ F(w, x, y, z) = \sum(2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$$




$$F = xz + wx' + x'y$$
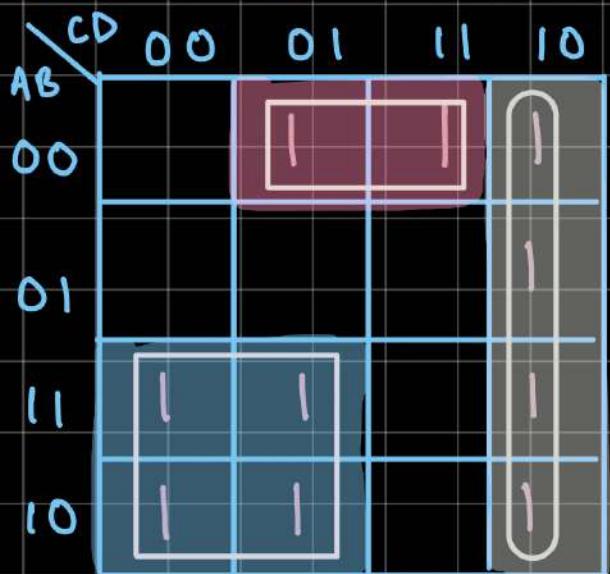
$$⑰ F(A, B, C, D) = \sum(1, 2, 3, 6, 8, 9, 10, 12, 13, 14)$$



$$F = CD' + A'B'D + AC'$$

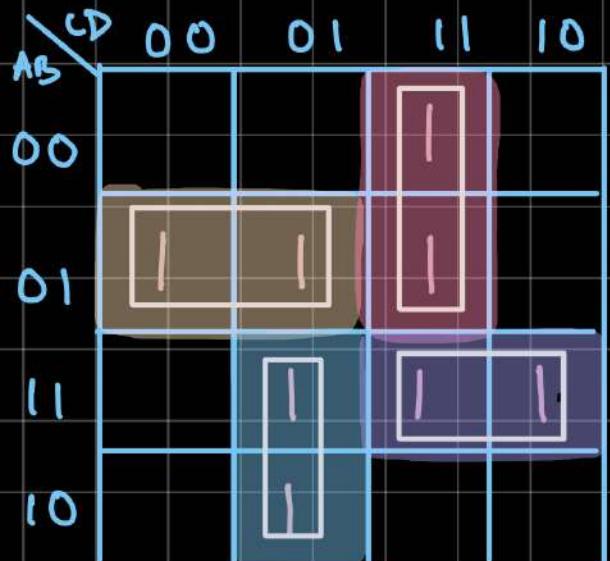
$$⑱ F(A, B, C, D) = \sum(3, 4, 5, 7, 9, 13, 14, 15)$$



$$F = AC'D + A'B'C' + A'C'D + ABC$$


→ Quad not considered as lesser number of implicants preferred

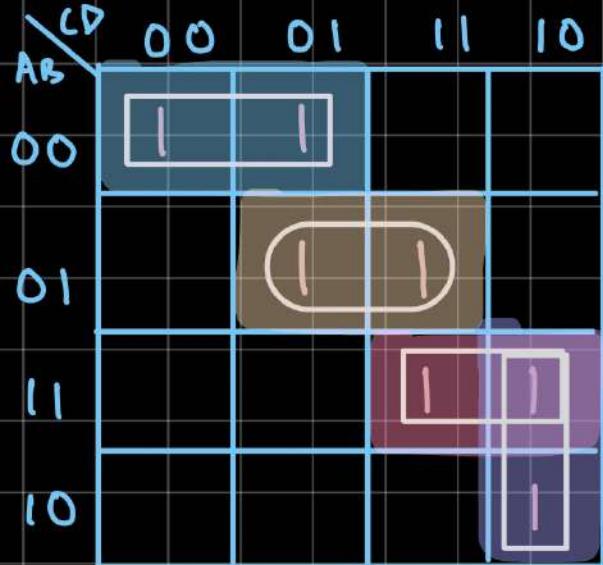19) $F(A, B, C, D) = \sum(0, 1, 5, 7, 15, 14, 10)$




$$F = \bar{A}\bar{B}C' + A'\bar{B}D + AB\bar{C} + ACD'$$

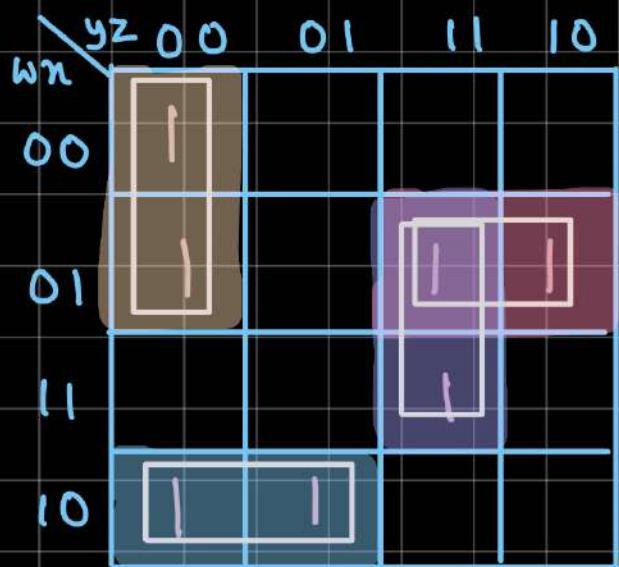20) $F(w, x, y, z) = \sum(0, 4, 6, 7, 8, 9, 15)$



$$F = w'y'z' + w\bar{x}y' + xy\bar{z} + w'xy$$

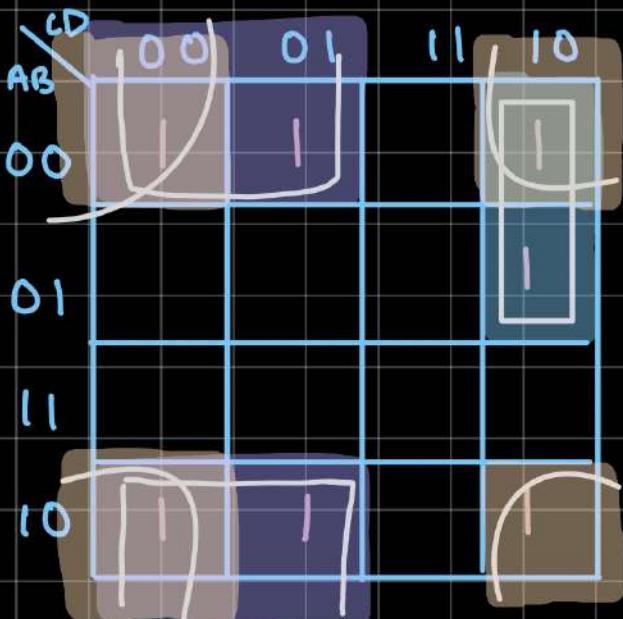21) $F = A'B'C' + B'CD' + A'BCD' + AB'C'$



$$\begin{aligned}
 F &= A'B'C'D + A'B'C'D' \\
 &\quad + AB'C'D' + A'B'CD' \\
 &\quad + A'BCD' + AB'C'D \\
 &\quad + AB'C'D' \\
 &= m_1 + m_0 + m_{10} + m_2 \\
 &\quad + m_6 + m_9 + m_8 \\
 &= \sum(0, 1, 2, 6, 8, 9, 10)
 \end{aligned}$$

$$\begin{aligned}
 &= B'C' + A'CD' \\
 &\quad + B'D'
 \end{aligned}$$

PRODUCT OF SUMS

- Group all 0's to obtain F'
- Apply complement to F' to obtain POS [DeMorgan]
- *→ Max terms imply the 0's [$\Pi(\cdot)$]

① Express the following in POS form

$$F(A, B, C, D) = \sum(0, 1, 2, 5, 8, 9, 10)$$

		CD	00	01	11	10
		AB	00	01	11	10
00	01	1	1	0	1	
		0	1	0	0	
11	10	0	0	0	0	
		1	1	0	1	

$$F' = BD' + CD + AB$$

$$\text{POS} = F = (F')'$$

$$F = (B' + D)(C' + D')(A' + B')$$

② POS for $F(x, y, z) = \Pi(0, 2, 5, 7)$

		yz	00	01	11	10
		x	0	0	0	0
0	1	0	0			
		1	0	0		

$$F' = x'y' + xz$$

$$\text{POS} = F = (x+y) \cdot (x'+z')$$

③ Write the TT for $F(x, y, z) = \sum m(1, 3, 4, 6)$ & solve for POS and SOP using kmap

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

		yz	00	01	11	10
		x	0	0	1	1
0	1	0	0	1	1	0
		1	1	0	0	1

$$\text{SOP: } F = x'z + xz'$$

$$\text{POS: } F' = x'z' + xz$$

$$F = (x+z) \cdot (x'+z')$$

DON'T CARE CONDITIONS

under specific conditions function is equal to 1,
otherwise 0.

Denoted by X

- ① Simplify the Boolean fn $F(w, x, y, z) = \sum(1, 3, 7, 11, 15)$
with DCC $d(w, x, y, z) = \sum(0, 2, 5)$

w\nx\yz	00	01	11	10
00	X	1	1	X
01	X	1		
11			1	
10			1	

$$F = w'x' + yz$$

* Quad not necessary
since all 1's are grouped

- ② $F(w, x, y, z) = \sum(1, 3, 7, 11, 15) + d(1, 2, 5)$

w\nx\yz	00	01	11	10
00		1	1	X
01	X			
11			1	
10			1	

$$F = yz + w'z$$

- ③ $F(w, x, y, z) = \sum(4, 5, 6, 7, 12) + d(0, 8, 13)$

w\nx\yz	00	01	11	10
00	X			
01	1	1	1	1
11	1	X		
10	X			

$$F = w'x + y'z'$$

$$④ F(w, x, y, z) = \sum(0, 1, 2, 4, 5, 7, 10) + d(3, 8, 15)$$

w\nx	yz	00	01	11	10
00		1	1	X	1
01		1	1	1	
11				X	
10		X		1	

$$F = w'y' + w'x' + yz$$

$$⑤ F(w, x, y, z) = \sum(2, 4, 5, 13, 15) + d(8, 9, 10, 11)$$

w\nx	yz	00	01	11	10
00					1
01		1	1		
11			1	1	
10		X	X	X	X

$$F = w'xy' + wz + x'yz'$$

$$⑥ F(x, y, z) = \sum(1, 3) + d(5, 6, 7)$$

x	yz	00	01	11	10
0			1	1	
1			X	X	X

$$f = \Sigma$$

NAND & NOR IMPLEMENTATION

NAND:



AND-invert



invert-OR

MULTILEVEL CIRCUIT FOR NAND

AND \rightarrow AND-invert

OR \rightarrow invert-OR

Complement input literal or add a bubble
when necessary

NOR



OR-invert



invert-AND

MULTILEVEL to NOR


OR \rightarrow OR-invert

AND \rightarrow invert-AND

① Build an AND and OR gate using NAND gates





[AND]

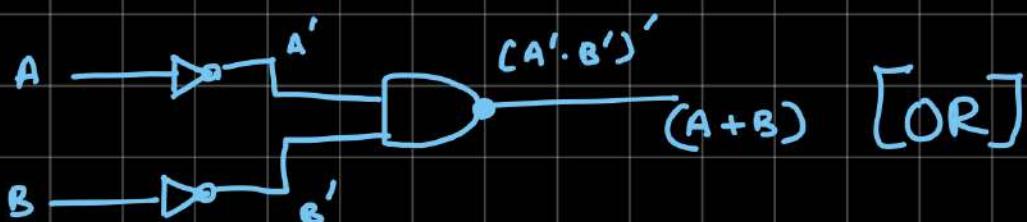


[OR]

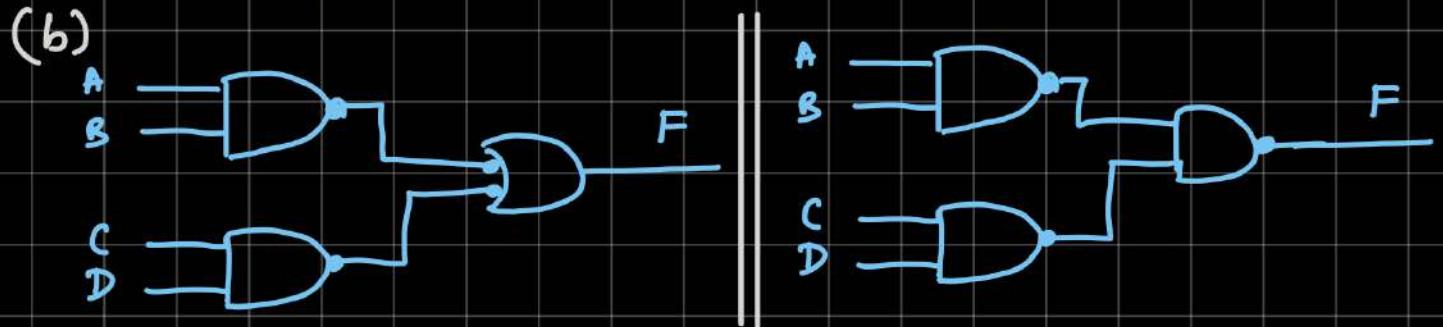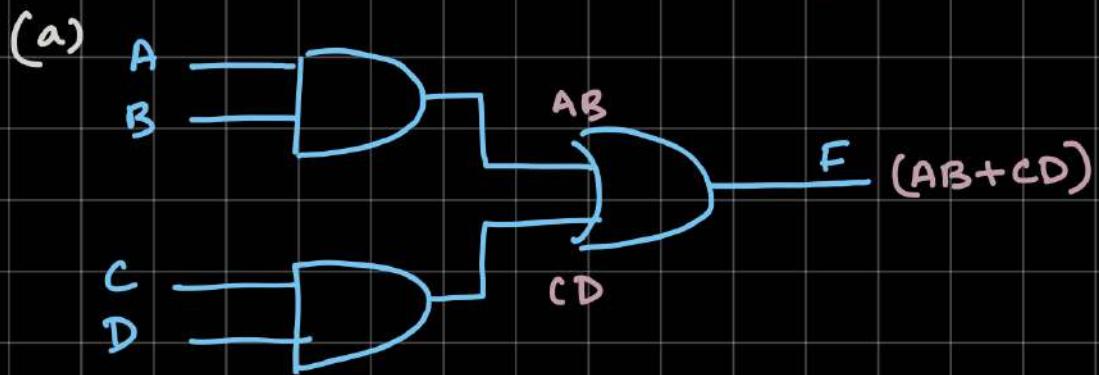② Implement $F = AB + CD$ (a) using AND and OR gate
 (b) using NAND gate




③ Implement the following Boolean function with NAND gates


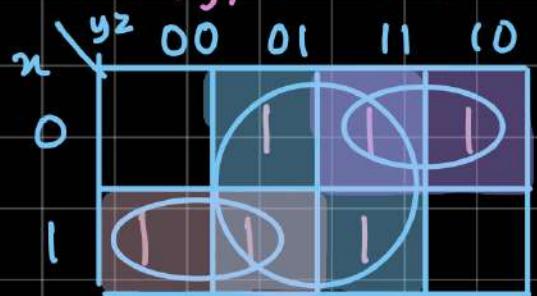
$$F(x, y, z) = (1, 2, 3, 4, 5, 7) \text{ using AND-i, i-OR}$$



$$F = z + x'y + xy'$$

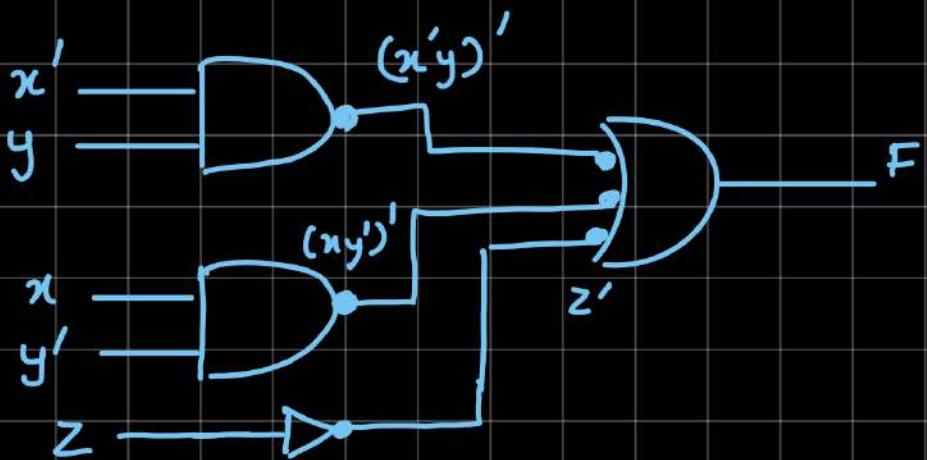

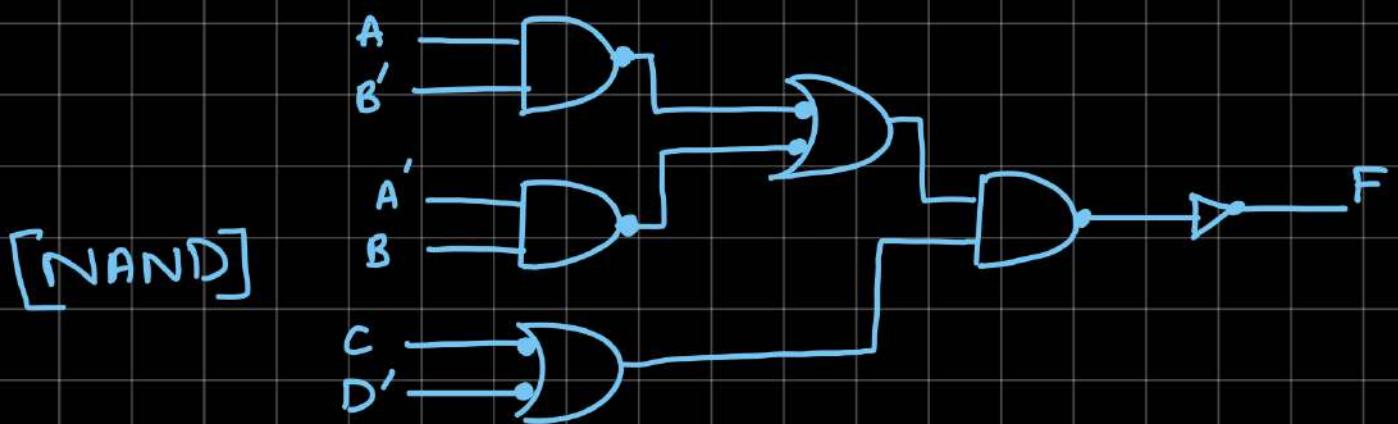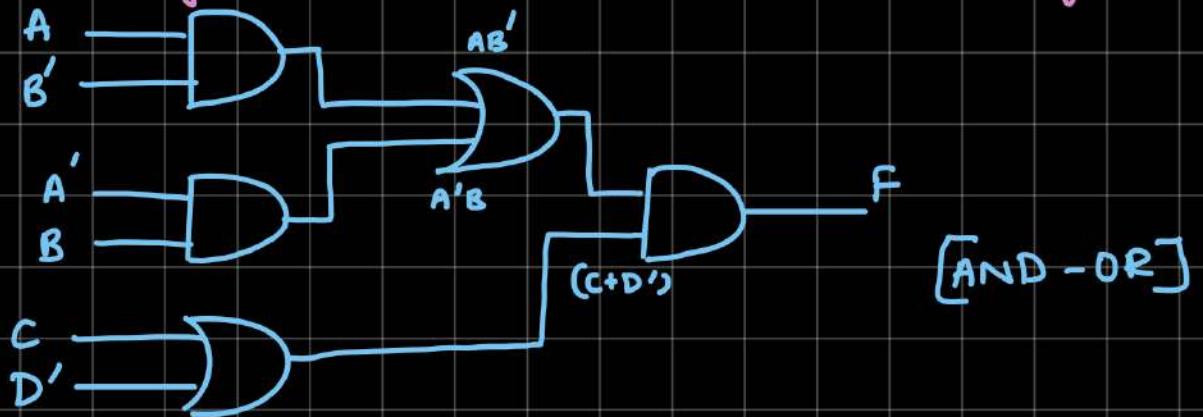
④ Implementing $F = (AB' + A'B)(C + D')$ using NAND




⑤ $F = A(CD + B) + BC'$ using NAND

$$F = ACD + AB + BC'$$


wiring AND-OR:

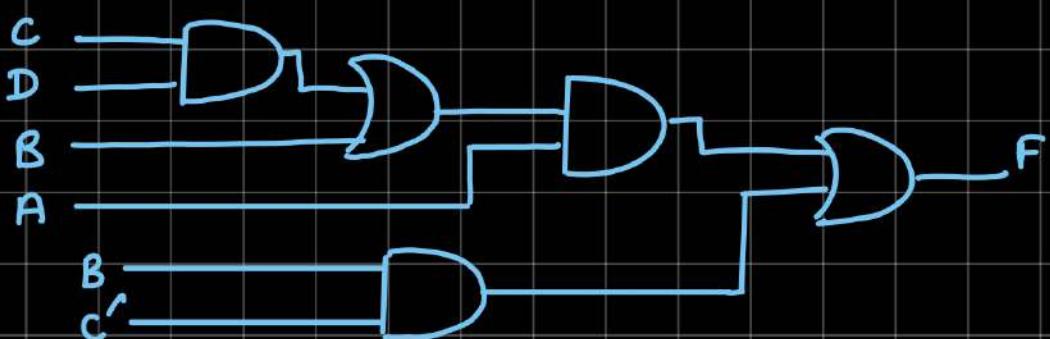


wiring NAND:

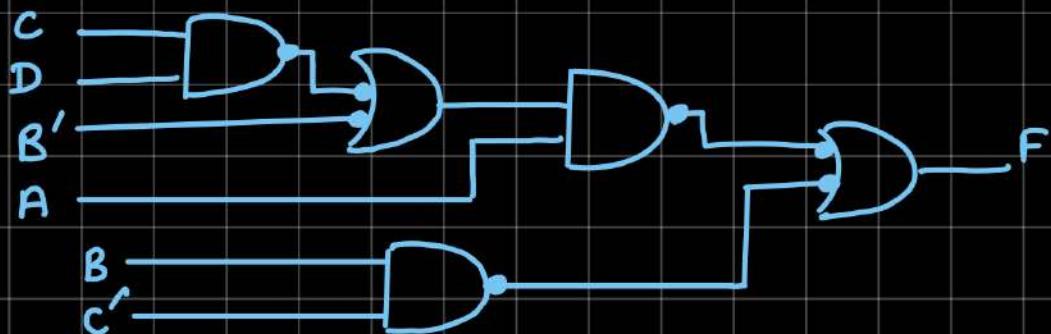

⑥ $F = (A+B)(C+D)E$ using NOR gates

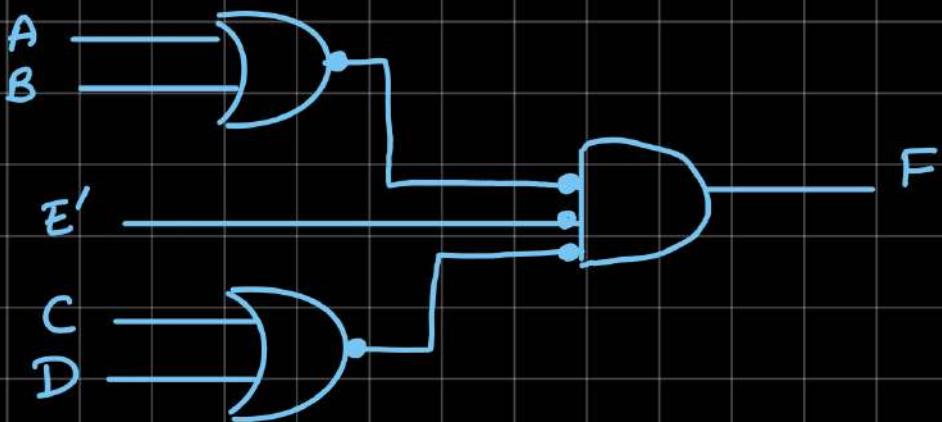


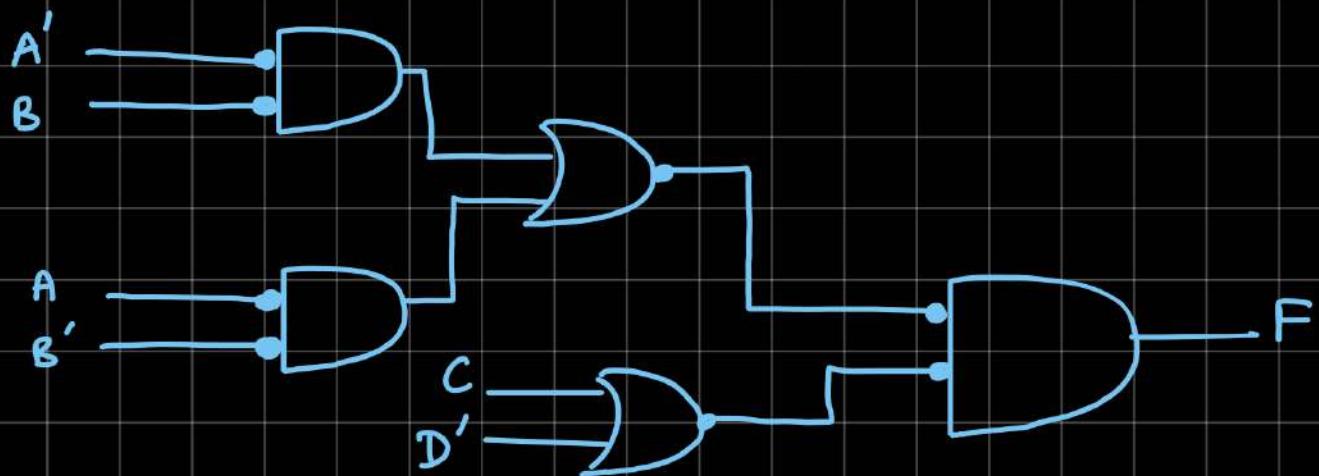⑦ $F = (AB' + A'B)(C + D')$ using NOR gates




OTHER TWO-LEVEL IMPLEMENTATION

→ WIRED LOGIC

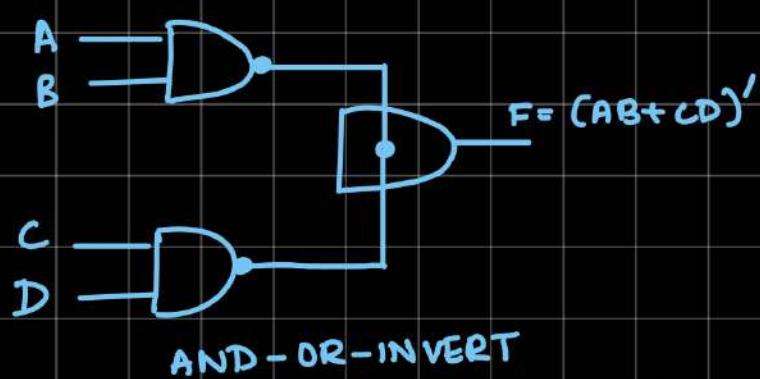

Wired-AND logic with 2NAND
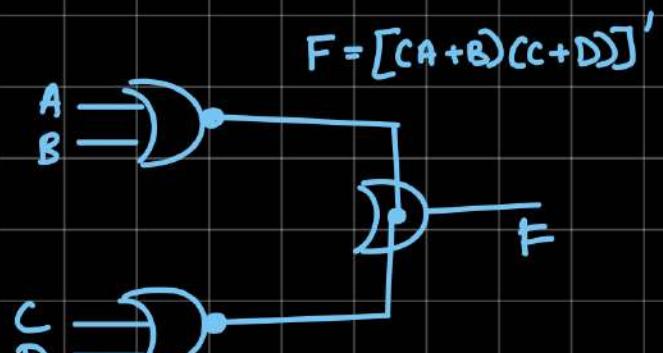
$$\begin{aligned} F &= (AB)' \dots (CD)' = (AB + CD)' \\ &= (A' + B')(C' + D') \end{aligned}$$



OR-AND- INVERT
Wired-OR in emitter-coupled logic gates

$$\begin{aligned} F &= (A+B)' + (C+D)' \\ &= [(A+B)(C+D)]' \end{aligned}$$

NONDEGENERATE FORMS

one gate for first level and another for second level
16 possible combinations

- 8 are degenerate as they degenerate into a single operation
- 8 nondegenerate are used to produce SOP & POS

8 NONDEGENERATE FORMS:

AND-OR

NAND-NAND

NOR-OR

OR-NAND

OR-AND

NOR-NOR

NAND-AND

AND-NOR

EQUIVALENT
NONDEGENERATE

(a)

(b)

Implements
the fn

Simplify
 F'

To get
Output

AND-NOR

NAND-AND

AND-OR-I

SOP by
combining
0's

F

OR-NAND



NOR-OR

OR-AND-I


POS by
combining 1's
& complementing

F


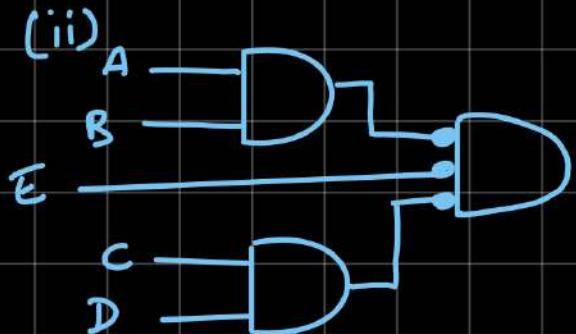
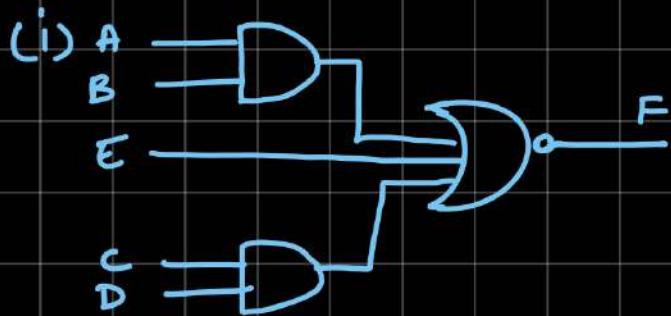
① Implement the following function $F = (AB + CD + E)'$ using (i) AND-OR-invert (ii) AND-invert-AND
 (iii) NAND-AND



(iii)

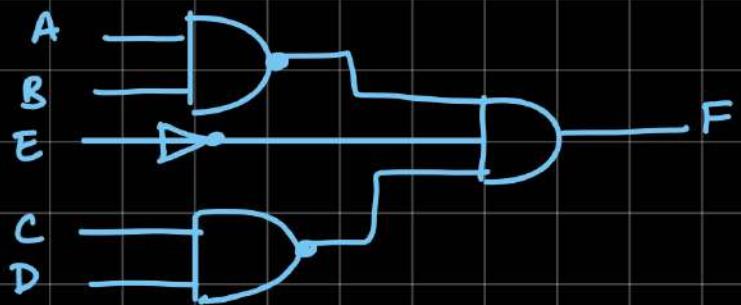

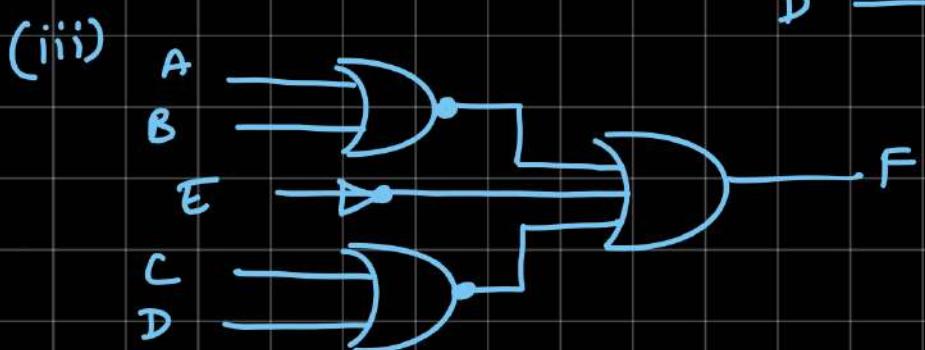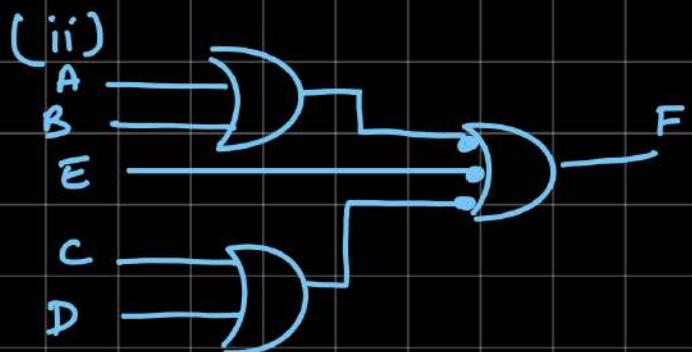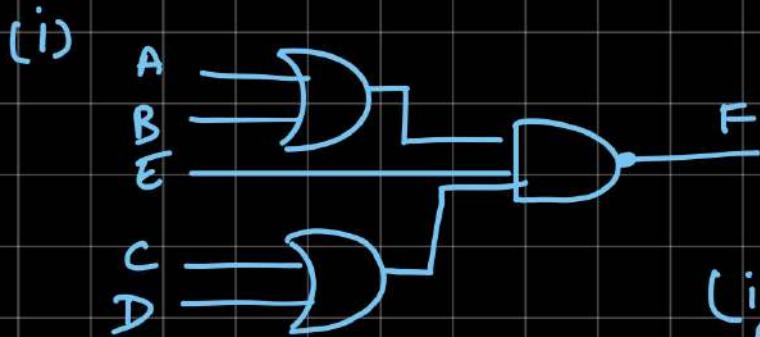② Represent the following function $F = [(A+B)(C+D)\bar{E}]'$ using (i) OR-AND-invert (ii) OR-invert-OR
 (iii) NOR-OR



③ Implement $f(x, y, z) = M(0, 6)$ with the four 2-level forms. Write SOP & F' form


$x \backslash yz$	00	01	11	10
0	1	0	0	0
1	0	0	0	1

$$F = x'y'z' + xyz' \rightarrow \text{SOP}$$


$$F' = xy' + z + x'y$$

$$\text{POS: } F = (x+y)(z')(x+y')$$


AND - NOR

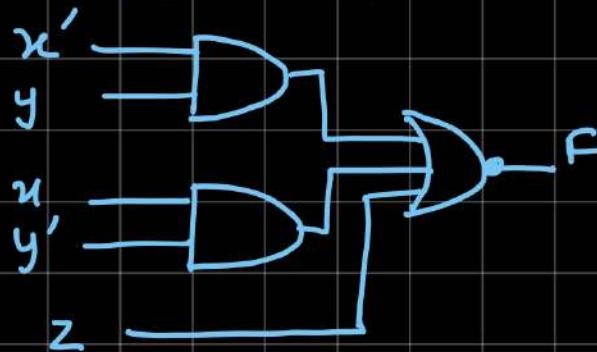


NAND-AND

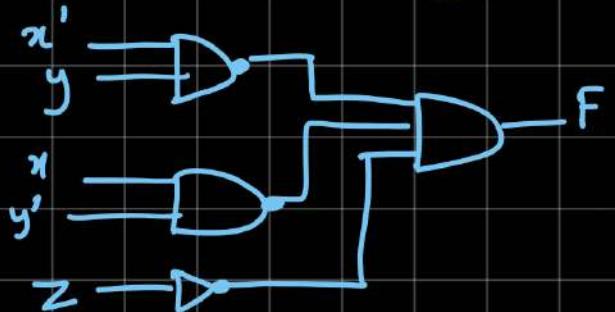

OR - NAND

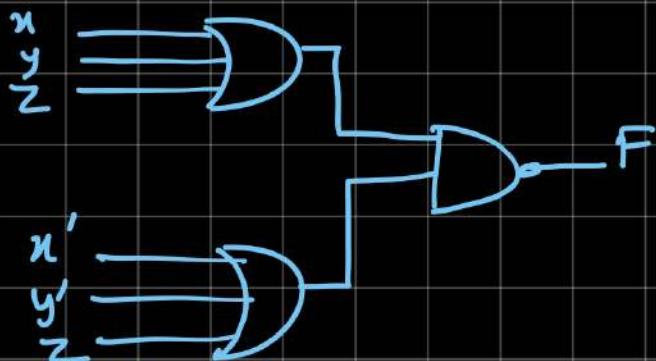

NOR - OR

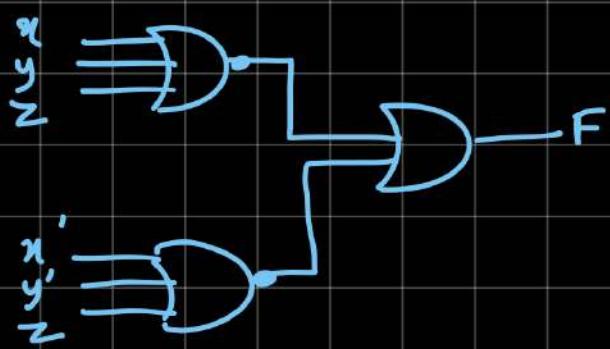

EXCLUSIVE - OR FUNCTION (XOR)

$$x \oplus y = xy' + x'y$$

x	y	$x \oplus y$
0	0	0
0	1	1
1	0	1
1	1	0


$$x \oplus 0 = x$$

$$x \oplus 1 = x'$$

$$x \oplus x = 0$$

$$x \oplus x' = 1$$
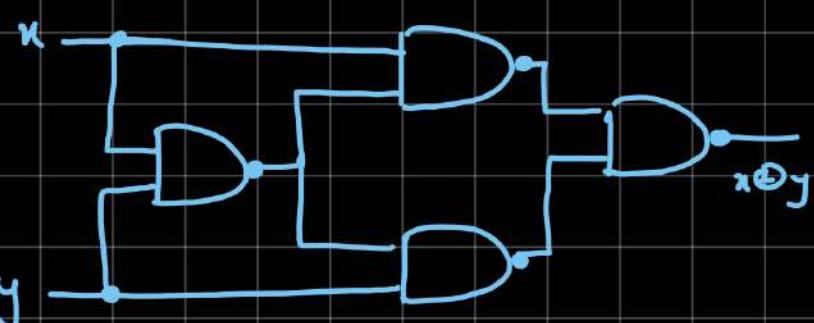
$$x \oplus y' = x' \oplus y = (x \oplus y)'$$



ODD FUNCTION

↳ odd parity
↳ odd no. of 1's

$$A \oplus B \oplus C$$

$$\text{Even fn} \rightarrow (A \oplus B \oplus C)'$$

Identify the minterms for odd & even functions for 3 variables

A	B\ C	00	01	11	10
0			1		1
1		1		1	

odd fn

$$F = A \oplus B \oplus C$$



$$= \Sigma(1, 2, 4, 7)$$

A	B\ C	00	01	11	10
0		1		1	
1			1		1

even fn

$$F = (A \oplus B \oplus C)'$$

$$= \Sigma(0, 3, 5, 6)$$

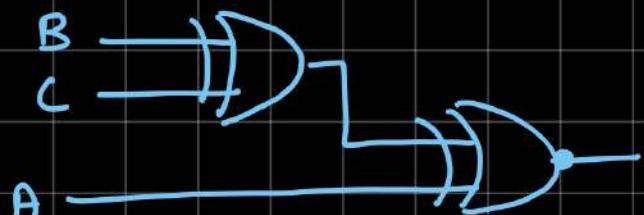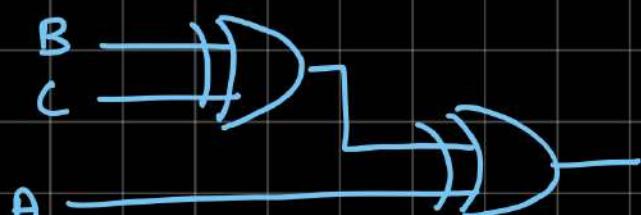

Identify the minterms for odd & even functions for 4 variables

	CD	00	01	11	10
O	AB	00	1	1	
D	01	1	1		
D	11	1	1	1	
I	10	1	1	1	

$$F = A \oplus B \oplus C \oplus D \\ = \Sigma(1, 2, 4, 7, 8, 11, 13, 14)$$

	CD	00	01	11	10
E	AB	00	1	1	
V	01		1	1	
E	11	1		1	
N	10		1	1	

$$F = (A \oplus B \oplus C \oplus D)' \\ = \Sigma(0, 3, 5, 6, 9, 10, 12, 15)$$

PARITY GENERATION & CHECKING

- Exclusive OR for error detection & correction
- parity bit → extra bit passed with message to make 1's even/odd.

Circuit that generates parity bit → parity generator
 Circuit that checks the parity → parity checker


EVEN PARITY GENERATOR

THREE BIT MESSAGE			P
X	Y	Z	
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Make the total no. of 1's even.

3-bit even-parity generator:


(XOR)

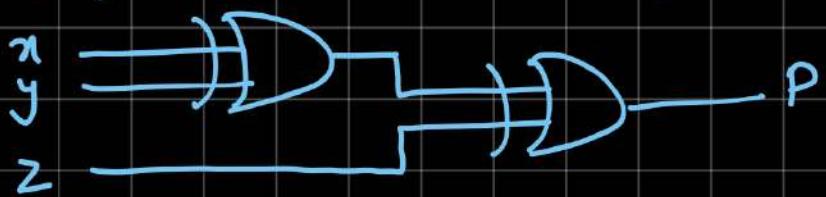

EVEN PARITY CHECKER

FOUR BITS RECEIVED				PARTY ERROR CHECKER
X	Y	Z	P	C
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

4-bit-even parity checker

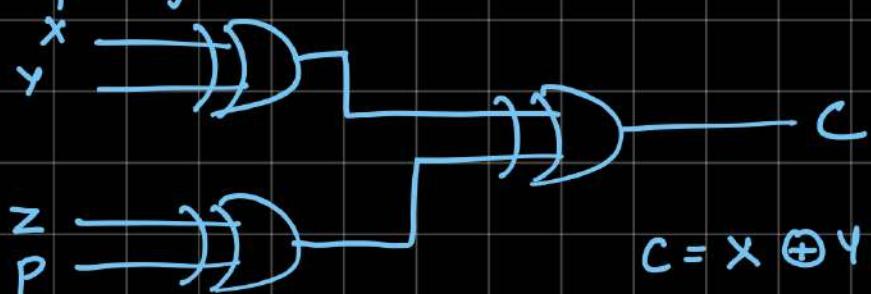


$$C = X \oplus Y \oplus Z \oplus P$$

ODD PARITY GENERATOR


$$P = X \oplus Y \oplus Z$$

THREE BIT MESSAGE			PARITY BIT
X	Y	Z	P
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

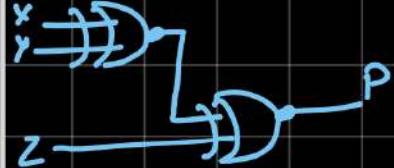

ODD PARITY CHECKER $C = X \oplus Y \oplus Z \oplus P$

FOUR BITS RECEIVED				PARITY ERROR CHECKER C
X	Y	Z	P	C
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

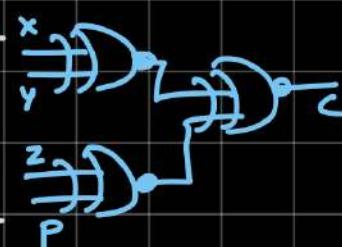

Logic circuits  Combination circuit
Sequential circuit — uses storage element

COMBINATIONAL CIRCUITS

↳ output depends on the inputs only

n input variable $\rightarrow 2^n$ input combination

n inputs & m outputs



→ ANALYSIS PROCEDURE

→ DESIGN PROCEDURE — CODE CONVERSION

Input \rightarrow 8 4 2 1 format


BCD — Binary coded decimal [0-9] + Rest are don't care

Excess 3 — "n+3"


CGray code — XOR b/w consecutive bit

Build a circuit to convert BCD code to excess 3-code


Decimal	BCD	excess 3 code
	A B C D	w x y z
0	0 0 0 0	0 0 1 1
1	0 0 0 1	0 1 0 0
2	0 0 1 0	0 1 0 1
3	0 0 1 1	0 1 1 0
4	0 1 0 0	0 1 1 1
5	0 1 0 1	1 0 0 0
6	0 1 1 0	1 0 0 1
7	0 1 1 1	1 0 1 0
8	1 0 0 0	1 0 1 1
9	1 0 0 1	1 1 0 0

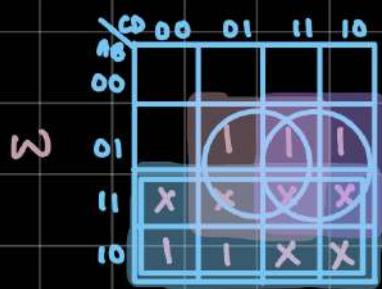


$$w = A + BD + BC \\ = A + B(C+D)$$

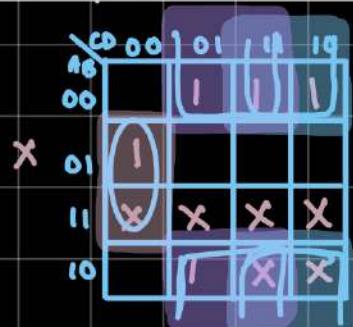

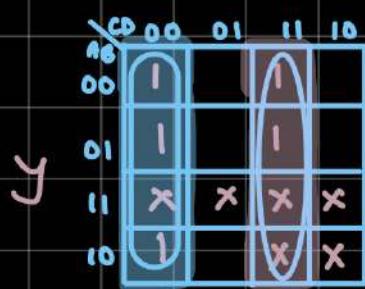
$$x = BC'D' + B'C + B'D \\ = B'(C+D) + B(C+D)'$$



$$y = C'D' + CD \\ = CD + (C+D)'$$

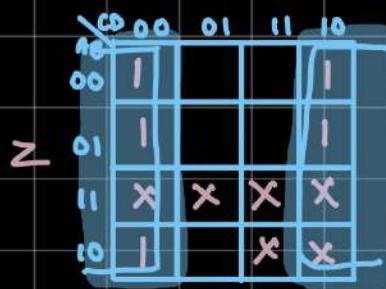

$$z = D'$$

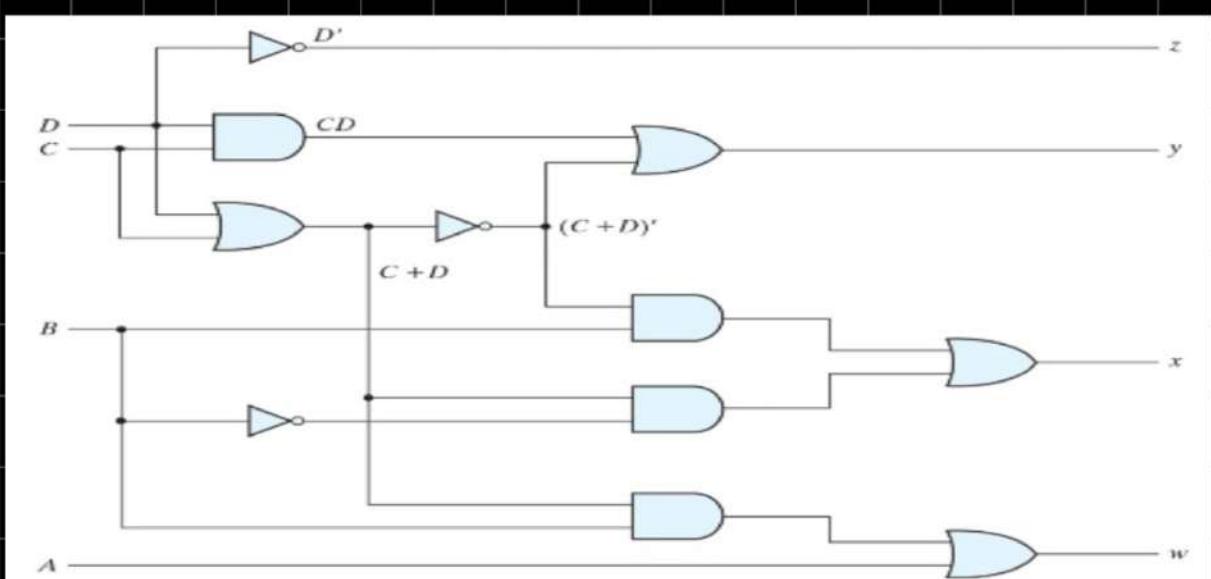

Convert 8 4 -2 -1 to excess 3 code

Decimal	8 A	4 B	-2 C	-1 D	excess 3 code w x y z
0	0	0	0	0	0011
1	0	1	1	1	0100
2	0	1	1	0	0101
3	0	1	0	1	0110
4	0	1	0	0	0111
5	1	0	1	1	1000
6	1	0	1	0	1001
7	1	0	0	1	1010
8	1	0	0	0	1011
9	1	1	1	1	1100

	CD AB	00	01	11	10
AB		0	x	x	x
00	0	0	0	0	0
01	0	0	0	0	0
11	x	x	1	x	x
10	1	1	1	x	x

w:

$$w = A$$

x:

	CD AB	00	01	11	10
AB		0	x	x	x
00	0	0	0	0	0
01	1	1	1	1	1
11	x	x	0	x	x
10	0	0	0	0	0

$$x = \bar{A}B$$

y:

	CD AB	00	01	11	10
AB		1	x	x	x
00	1	1	0	0	0
01	1	1	0	0	0
11	x	x	0	x	x
10	1	1	0	0	0

$$y = \bar{C}$$

z:

	CD AB	00	01	11	10
AB		1	x	x	x
00	1	1	0	0	1
01	1	0	0	0	1
11	x	x	0	x	x
10	1	0	0	0	1

$$z = \bar{D}$$

Convert BCD to Gray code

Decimal	BCD	GRAY CODE
	A B C D	W X Y Z
0	0 0 0 0	0 0 0 0
1	0 0 0 1	0 0 0 1
2	0 0 1 0	0 0 1 1
3	0 0 1 1	0 0 1 0
4	0 1 0 0	0 1 1 0
5	0 1 0 1	0 1 1 1
6	0 1 1 0	0 1 0 1
7	0 1 1 1	0 1 0 0
8	1 0 0 0	1 1 0 0
9	1 0 0 1	1 1 0 1
10	1 0 1 0	1 1 1 1
11	1 0 1 1	1 1 1 0
12	1 1 0 0	1 0 1 0
13	1 1 0 1	1 0 1 1
14	1 1 1 0	1 0 0 1
15	1 1 1 1	1 0 0 0

0010
 ↓↓↓↓
 0011
 BC
 XOR
 Gray

	CD	00	01	11	10
AB	00	0	0	0	0
00	01	0	0	0	0
01	11	1	1	1	1
10	11	1	1	1	1

w:

$$w = A$$

	CD	00	01	11	10
AB	00	0	0	0	0
00	01	1	1	1	1
01	11	0	0	0	0
10	11	1	1	1	1

x:

$$\begin{aligned}
 x &= \bar{A}B + A\bar{B} \\
 &= A \oplus B
 \end{aligned}$$

	CD	00	01	11	10
AB	00	0	0	1	1
00	01	1	1	0	0
01	11	1	0	0	0
11	11	0	0	0	0
10	11	0	0	0	0

y:

$$\begin{aligned}
 y &= \bar{A}\bar{B}C + B\bar{C} \\
 &\quad + A\bar{C}
 \end{aligned}$$

z:

	CD	00	01	11	10
AB	00	0	1	0	1
00	01	0	1	0	1
01	11	0	1	0	1
11	11	0	1	0	1
10	11	0	1	0	1

$$\begin{aligned}
 z &= \bar{C}D + C\bar{D} \\
 &= C \oplus D
 \end{aligned}$$



BINARY ADDERS

HALF ADDER

$$S = x'y + xy' = x \oplus y$$

$$C = xy$$

x	y	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

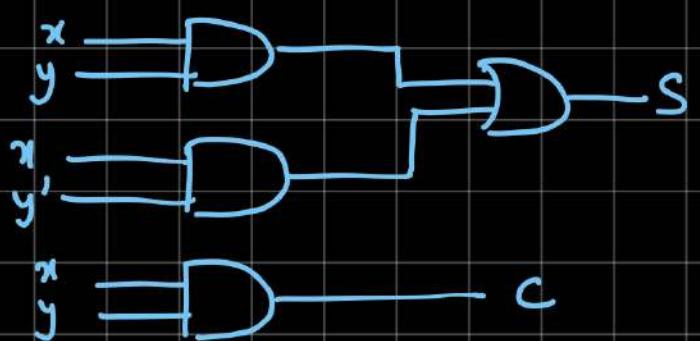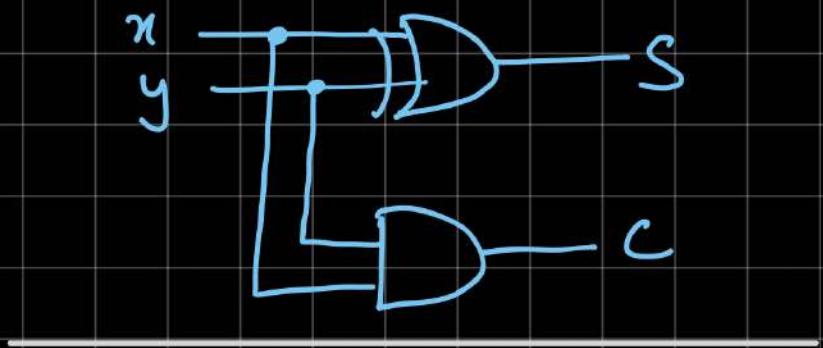

FULL ADDER

x	y	z	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


$$S = x'y'z + x'yz' + xy'z' + xyz \\ = x \oplus y \oplus z$$

$$C = xy + xz + yz \\ = (x \oplus y)z + xy$$

x	y	z	00	01	11	10
0	0	0	0	1	1	1
1	1	0	1	1	1	1
			0	1	1	1

S:

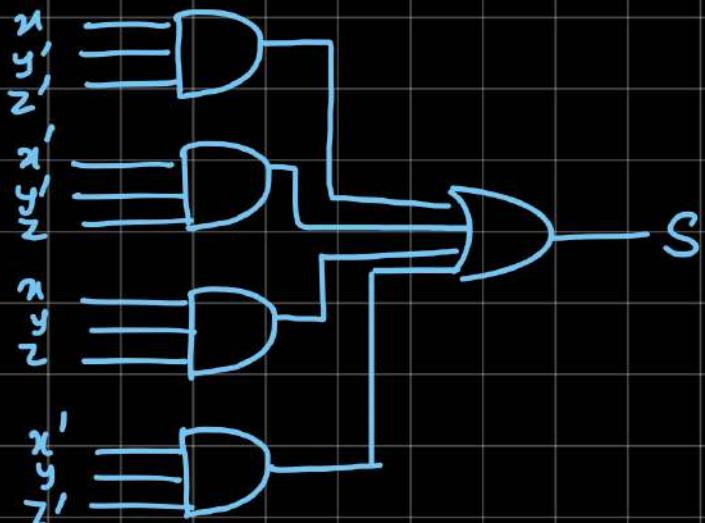
$$S = \bar{x}y'z' + x'y'z + \bar{x}yz + x'y'z'$$




x	y	z	00	01	11	10
0	0	0	0	1	1	1
1	1	0	1	1	1	1
			0	1	1	1

C:

$$C = \bar{x}y + \bar{x}z + yz$$

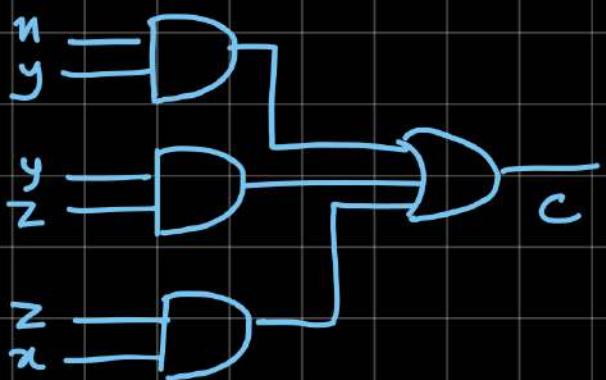


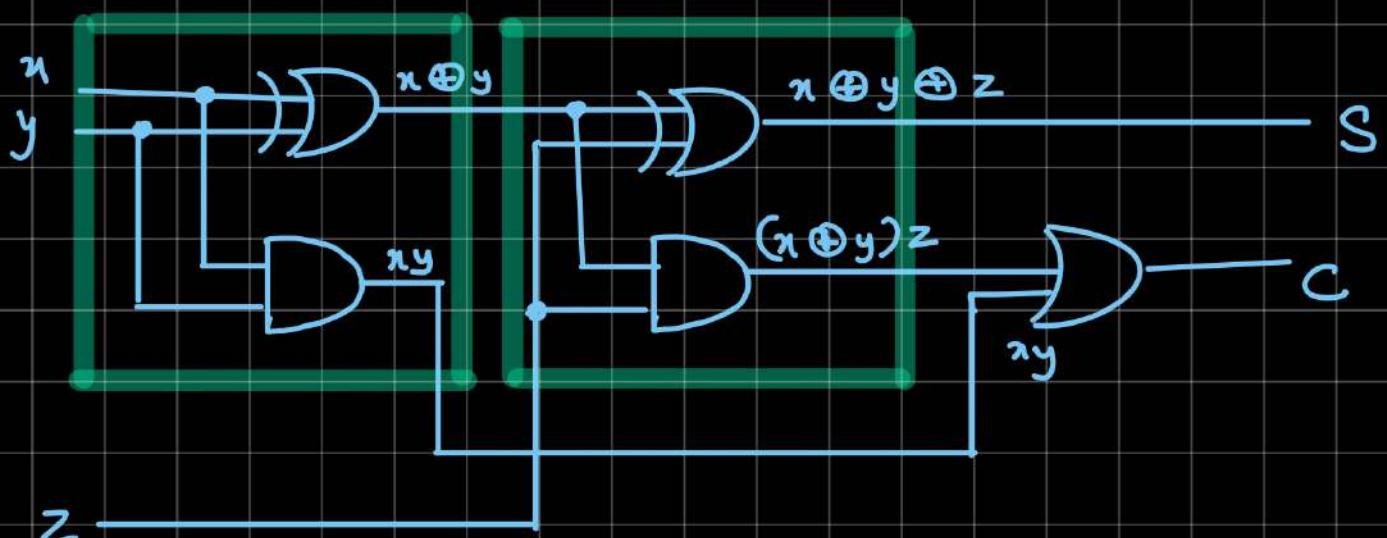Implement FULL ADDER with two HALF ADDERS




TYPES OF ADDERS

- RCA
- CLA
- Prefix adders

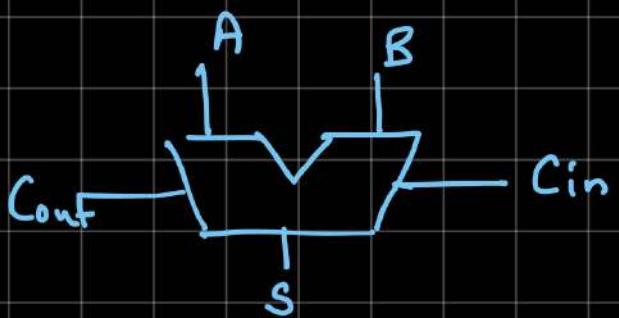

BINARY ADDER

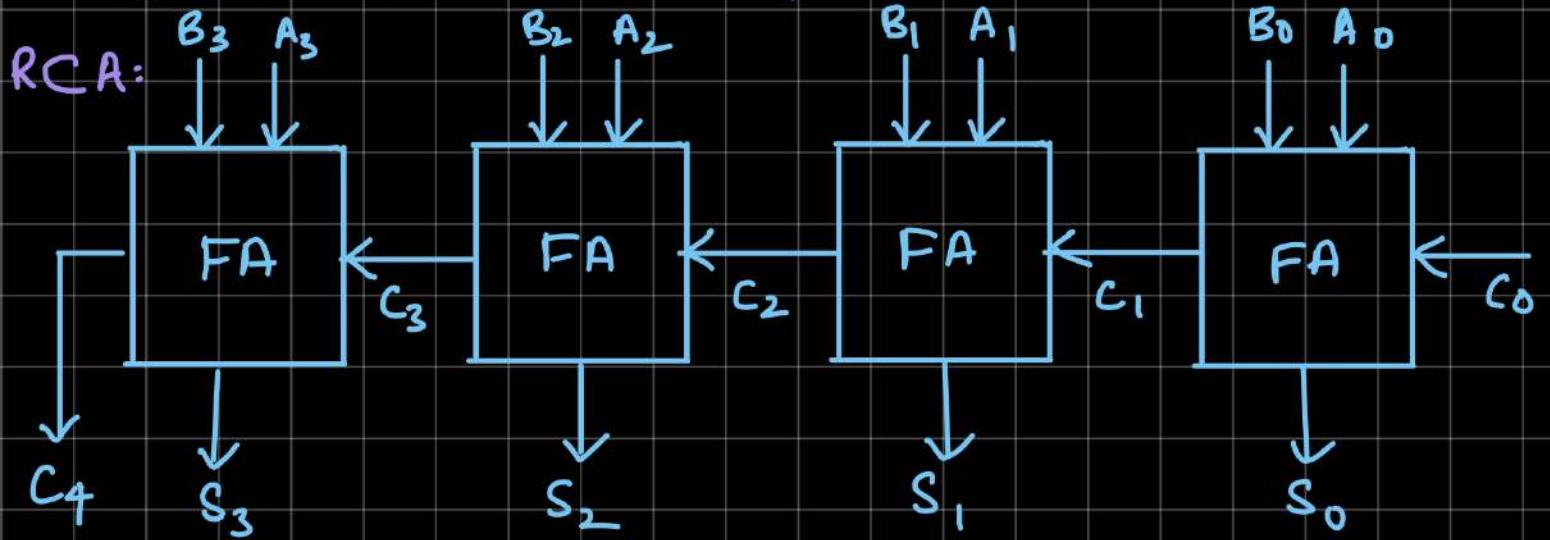


$$A = 1011 \quad \& \quad B = 0011$$

$$\text{tripple} = N t_{FA}$$

Subscript	3	2	1	0	RCA delay
Input carry	0	1	1	0	C_i
Augend	1	0	1	1	A_i
Addend	0	0	1	1	B_i
Sum	1	1	1	0	S_i
Output carry	0	0	1	1	C_{i+1}

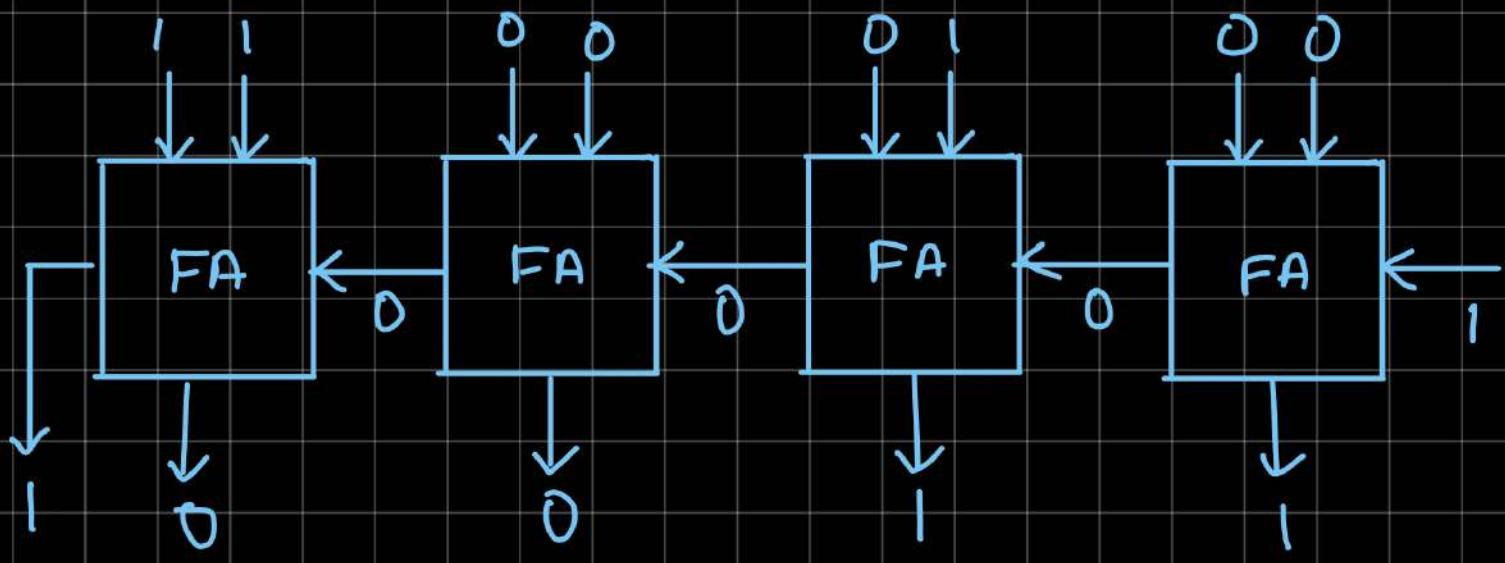Q. Realise the following addition using Ripple Carry Adder for input $A=1010 \ \& \ B=1000$. Consider $C_{in}=1$



CARRY LOOK AHEAD LOGIC

RCA is slow and follows a sequential chain
To overcome this, CLA is used where they are divided into blocks & solved parallelly

P_i → Carry propagate — whether carry will propagate to $i+1$ stage
 G_i → Carry generate — Produces carry of 1 if $A_i = 1 \& B_i = 1$

$$P_i = A_i \oplus B_i$$


$$G_i = A_i B_i$$

$$S_i = P_i \oplus C_i$$

$$\therefore S_i = x_i \oplus y_i \oplus c_i$$

$$C_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$C_{i+1} = G_i + P_i C_i$$

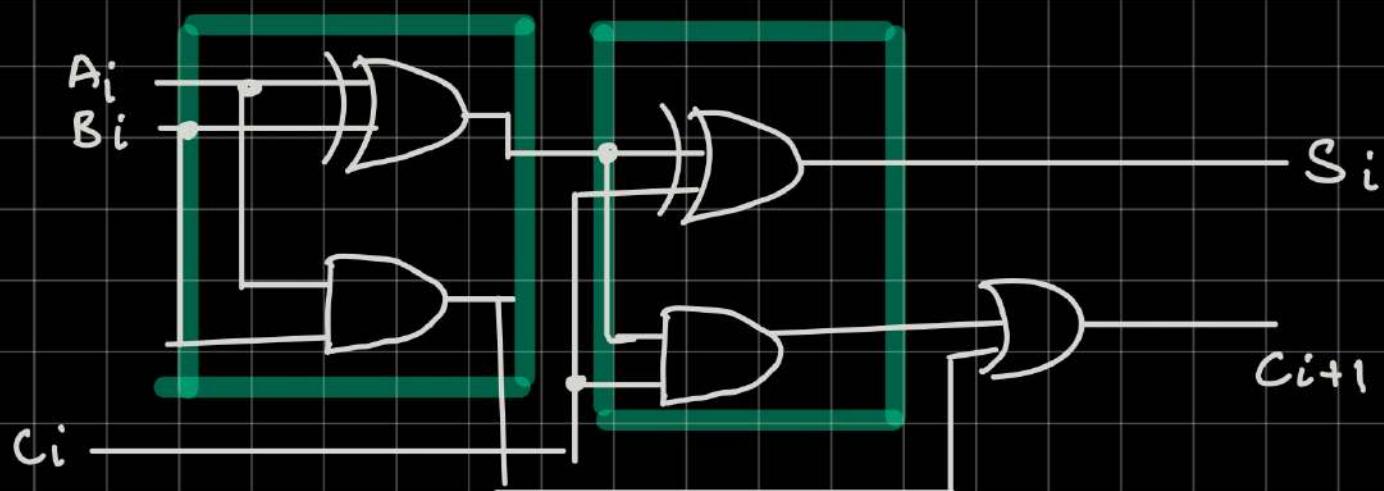

Given the value of C_0 , find the value of equation for C_3 and realise the given circuit


$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1$$

$$C_3 = G_2 + P_2 C_2$$

$$C_3 = G_2 + P_2 (G_1 + P_1 C_1) = G_2 + P_2 G_1 + P_2 P_1 C_1$$
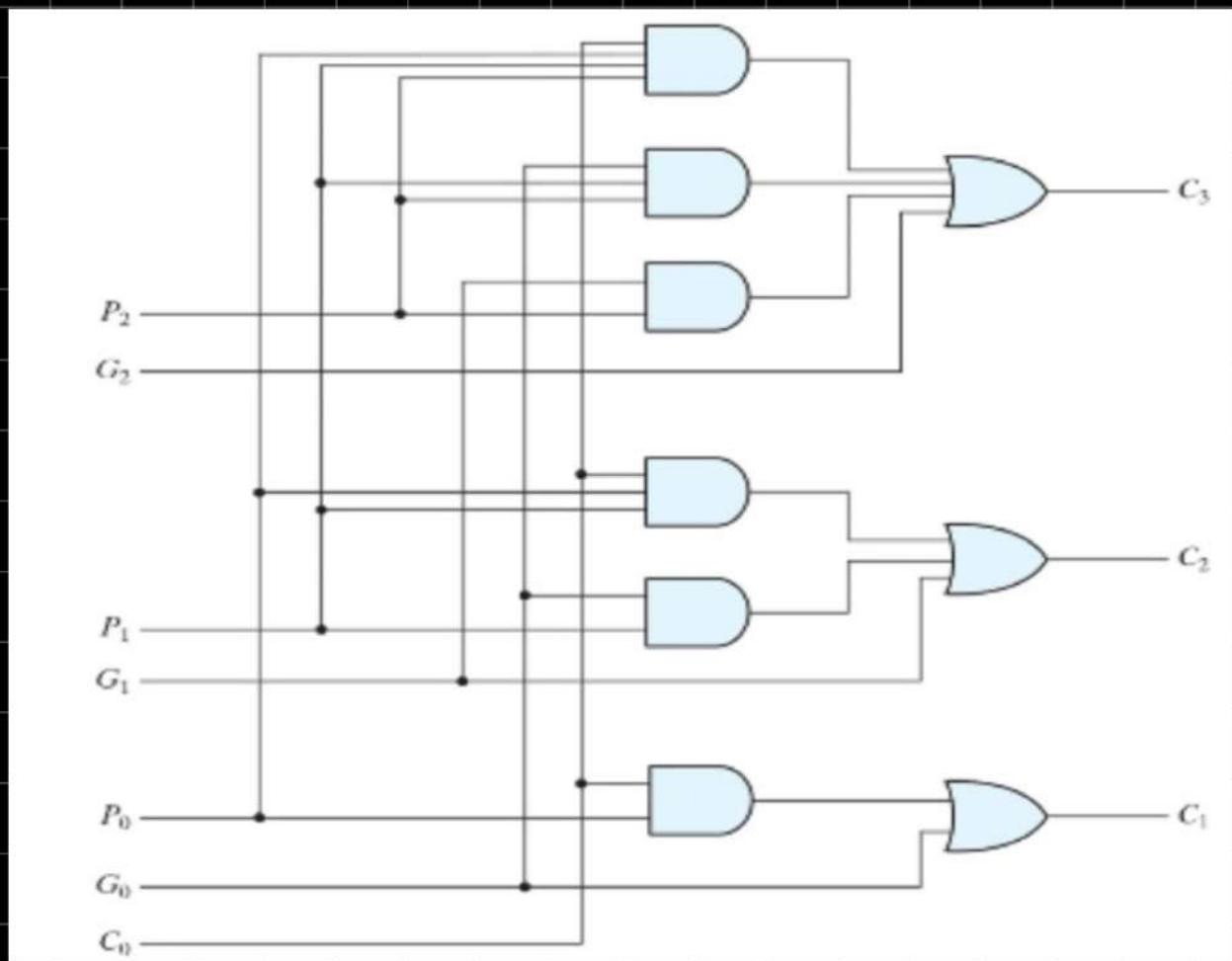
$$\begin{aligned}
 C_3 &= G_2 + P_2 G_1 + P_2 P_1 (G_0 + P_0 C_0) \\
 &= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0
 \end{aligned}$$



Implement addition of 2 binary numbers 1010 & 0001 show the calculation of S_0, S_1, S_2, S_3 & also calculate the carry at each stage. Find value of C_4 considering $C_0 = 1$

$$S_0 = P_0 \oplus C_0 = (0 \oplus 1) \oplus 1 = 0$$

$$C_1 = G_0 + P_0 C_0 = (0 \cdot 1) + (1 \cdot 1) = 1$$

$$S_1 = P_1 \oplus C_1 = (1 \oplus 0) \oplus 1 = 0$$

$$C_2 = G_1 + P_1 C_1 = (1 \cdot 0) + (1 \cdot 1) = 1$$

$$S_2 = P_2 \oplus C_2 = (0 \oplus 0) \oplus 1 = 1$$

$$C_3 = G_2 + P_2 C_2 = (0 \cdot 0) + (0 \cdot 1) = 0$$

$$S_3 = P_3 \oplus C_3 = (1 \oplus 0) \oplus 0 = 1$$

$$C_4 = G_3 + P_3 C_3 = (1 \cdot 0) + (1 \cdot 0) = 0$$

$$\begin{array}{r}
 & 011 \\
 & | \\
 1010 & + 0001 \\
 \hline
 & 1
 \end{array}$$

$$S = \underline{\underline{1100}}$$

BINARY SUBTRACTOR


HALF SUBTRACTOR:

A	B	D	B_0
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$D = \bar{A}B + A\bar{B}$$


$$= A \oplus B$$

$$B_0 = \bar{A} \cdot B$$

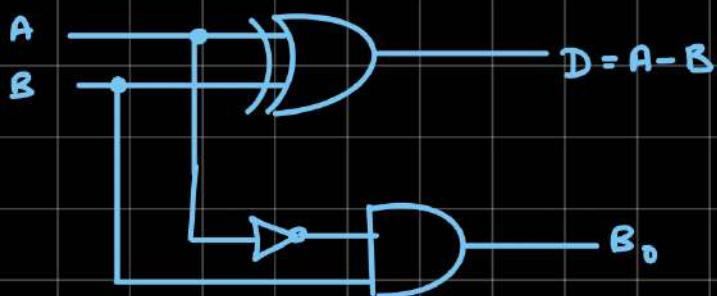

FULL SUBTRACTOR

Input			Output	
A	B	B_i	D	B_o
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

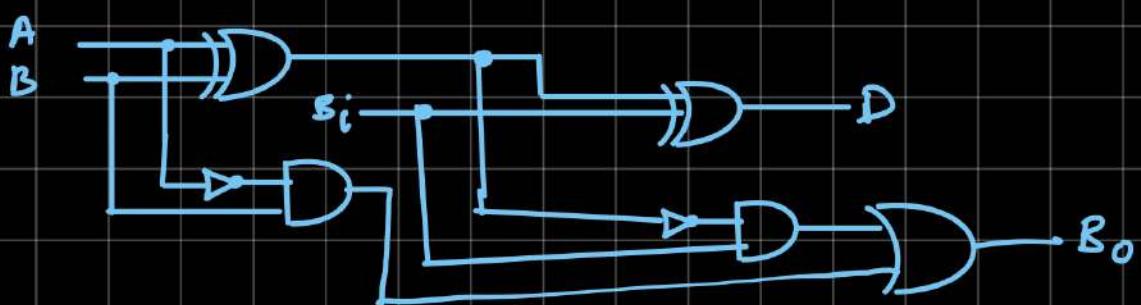

Build a 3-bit subtractor and represent in the form of circuit.

A	B	C	D	B_0
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

D:

C	AB	00	01	11	10
		0	1	1	1
C	AB	00	01	11	10
		0	1	1	1


B_0 :

C	AB	00	01	11	10
		0	1	1	1
C	AB	00	01	11	10
		1	1	1	1

$$\begin{aligned}
 D &= A'B'C + A'BC' \\
 &\quad + ABC + AB'C' \\
 &= A \oplus B \oplus C
 \end{aligned}$$

$$\begin{aligned}
 B_0 &= A'B + A'C \\
 &\quad + BC
 \end{aligned}$$

(Implement circuit)

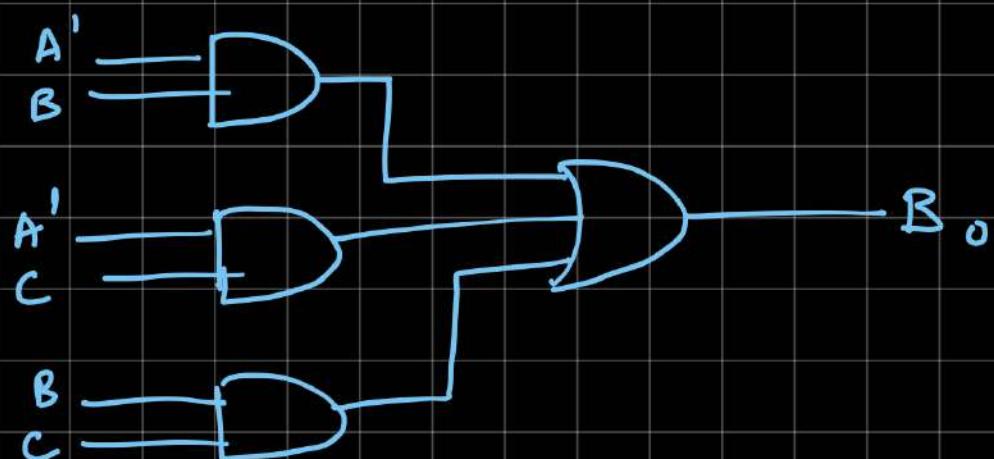

TWO'S COMPLEMENT



$$A - B = A + 2^k \text{ 's complement of } B$$

$$= A + 1^k \text{ 's complement of } B + 1$$

For unsigned, $A \geq B \Rightarrow A - B$

$A < B \Rightarrow 2^k \text{ 's complement of } (B - A)$

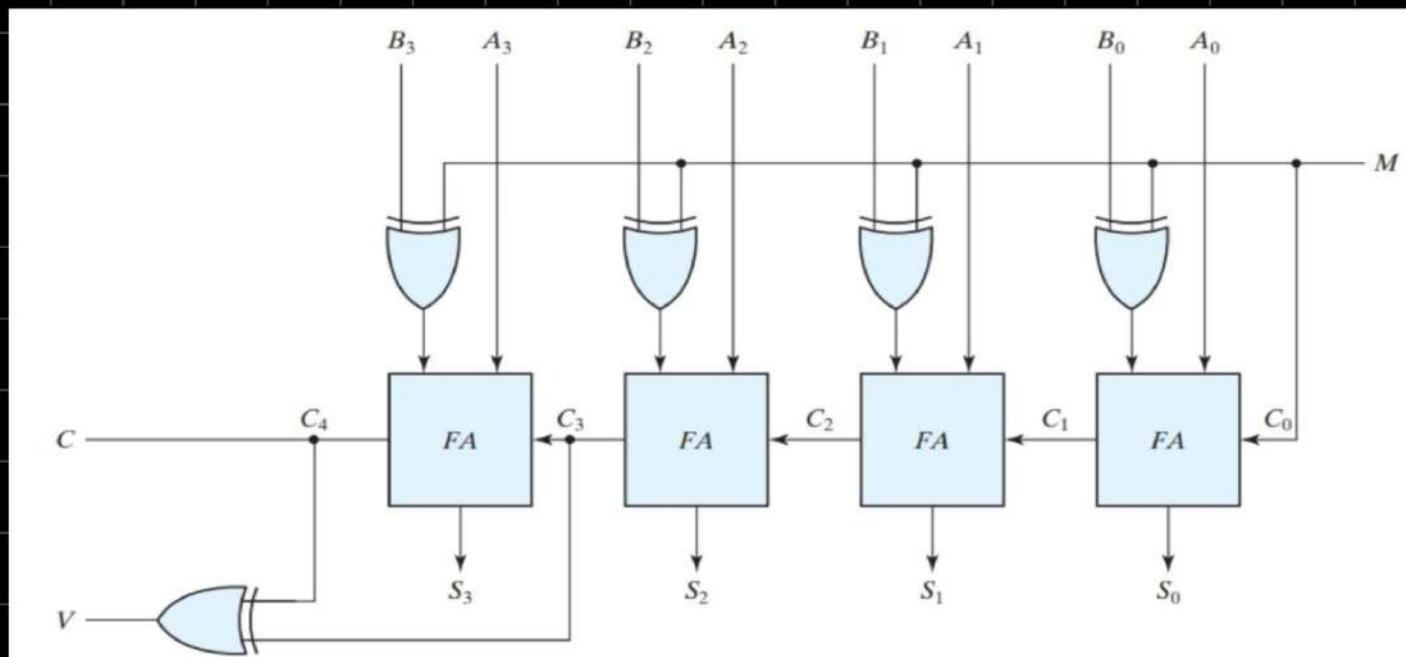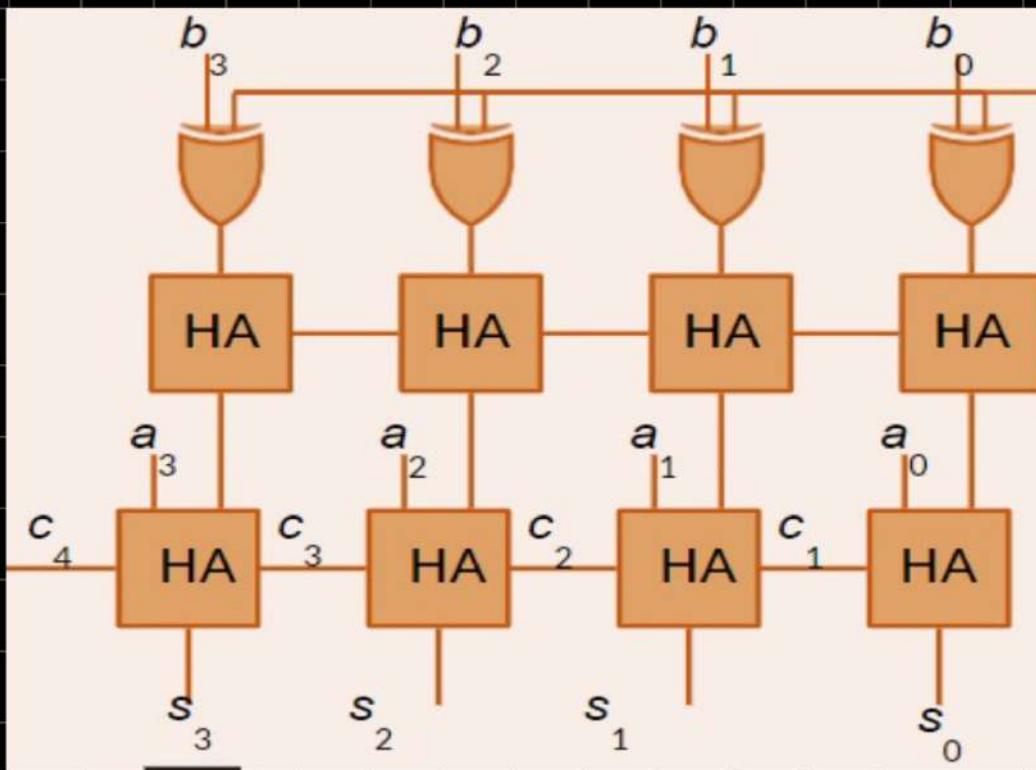For signed, $A - B \rightarrow \text{no overflow}$



OVERFLOW CONDITION

when two numbers with n digits each
are added and the sum is a number
occupying $n+1$ digits, overflow is detected

opp sign \rightarrow no OF
same sign \rightarrow OF

① Represent -2 using 2's complement

$$(-2) \Rightarrow 1010$$

$$\begin{array}{r} -2 \\ 1's \\ 2's \\ \hline 0110 \\ = 6 \end{array}$$

$$(+2) \Rightarrow 0010$$

$$\begin{array}{r} +2 \\ 1's \\ 2's \\ \hline 1110 \\ = -6 \end{array}$$

② Find the decimal value of 2's complement representation of the complement 1001

$$\begin{array}{r} 1001 \\ 1's \\ 2's \\ \hline 0111 \Rightarrow 7 \end{array}$$

③ Find $5-3$ using 2's complement

To find 2's complement of +3 \Rightarrow

$$\begin{array}{r} 5-3 \Rightarrow \\ 0101 \\ 1101 \\ \hline 0010 \end{array}$$

$$0010 \Rightarrow 2$$

$$\begin{array}{r} 0011 \\ 1's \\ 2's \\ \hline 1101 \end{array}$$

↓
2's complement of 3
replaces -3

$$5-3=2$$

- ④ Subtract (i) $-3 \& 7$ (iii) $-7 \& 5$
(ii) $6 \& 3$ (iv) $-7 \& +1$

$$(i) -3 \& 7$$

2's complement of +3 \Rightarrow

$$\begin{array}{r} 0011 \\ \text{l's} \quad 1100 \\ 2's \quad \frac{-1}{1101} \end{array}$$

2's complement of +7 \Rightarrow

$$\begin{array}{r} 0111 \\ \text{l's} \quad 1000 \\ 2's \quad \frac{-1}{1001} \end{array}$$

$$-3 - 7 \Rightarrow \begin{array}{r} 1101 \\ 1001 \\ \hline 10110 \end{array}$$

\rightarrow NA since out of range

$$(ii) 6 \& 3$$

2's complement of +3 \Rightarrow

$$\begin{array}{r} 0011 \\ \text{l's} \quad 1100 \\ 2's \quad \frac{-1}{1101} \end{array}$$

$$\begin{array}{r} 0110 \\ 1101 \\ \hline 10011 \end{array} \Rightarrow 3$$

$$(iii) -7 \& 5$$

2's complement of 5 \Rightarrow

$$\begin{array}{r} 0101 \\ \text{l's} \quad 1010 \\ 2's \quad \frac{-1}{1011} \end{array}$$

2's complement of +7 \Rightarrow

$$\begin{array}{r} 0111 \\ \text{l's} \quad 1000 \\ 2's \quad \frac{-1}{1001} \end{array}$$

$$-7 - 5 \Rightarrow \begin{array}{r} 11 \\ 1001 \\ \hline 10100 \end{array}$$

\Rightarrow out of range

(iv) -7 & 1

2's complement of 1 \Rightarrow

$$\begin{array}{r} \text{1's} \quad 0 \ 0 \ 0 \ 1 \\ \text{2's} \quad 1 \ 1 \ 1 \ 0 \\ \hline & \quad 1 \end{array} \quad \{$$

2's complement of +7 \Rightarrow

$$\begin{array}{r} \text{1's} \quad 0 \ 1 \ 1 \ 1 \\ \text{2's} \quad 1 \ 0 \ 0 \ 0 \\ \hline & \quad 1 \end{array} \quad \{$$

$$\begin{array}{r} 1 \ 1 \ 1 \\ 1 \ 0 \ 0 \ 1 \\ 1 \ 1 \ 1 \ 1 \\ \hline \end{array}$$

$$\begin{array}{r} 1 \ 0 \ 0 \ 0 \\ \hline = \quad 1 \ 0 \ 0 \ 1 \end{array} \rightarrow \text{overflow}$$

$\hookrightarrow 8$

DECIMAL ADDER - BCD

Add 6 to convert the number from Primary to
if it exceeds 9 $\quad \text{BCD} \quad (8421)$

Max allowed : $9 + 9 + 1 = 19 \rightarrow$ cannot exceed this sum

$45 + 28 \Rightarrow$

$$\begin{array}{r} & & 1 \\ & 0 & 1 & 0 & 0 & 0 & 1 & 0 & 1 \\ & 0 & 0 & 1 & 0 & 1 & 0 & 0 & 0 \\ \hline & 0 & 1 & 1 & 1 & 1 & 1 & 0 & 1 \\ + 6 & & & & & & 0 & 1 & 1 & 0 \\ \hline & 0 & 1 & 1 & 1 & 1 & 0 & 0 & 1 & 1 \end{array} \rightarrow \text{BCD sum}$$

$6 \Rightarrow 0110$

DECIMAL

BINARY SUM


BCD SUM

K Z₈ Z₄ Z₂ Z₁

C S₈ S₄ S₂ S₁

0	0 0 0 0 0	0 0 0 0 0
1	0 0 0 0 1	0 0 0 0 1
2	0 0 0 1 0	0 0 0 1 0
3	0 0 0 1 1	0 0 0 1 1
4	0 0 1 0 0	0 0 1 0 0
5	0 0 1 0 1	0 0 1 0 1
6	0 0 1 1 0	0 0 1 1 0
7	0 0 1 1 1	0 0 1 1 1
8	0 1 0 0 0	0 1 0 0 0
9	0 1 0 0 1	0 1 0 0 1
10	0 1 0 1 0	1 0 0 0 0
11	0 1 0 1 1	1 0 0 0 1
12	0 1 1 0 0	1 0 0 1 0
13	0 1 1 0 1	1 0 0 1 1
14	0 1 1 1 0	1 0 1 0 0
15	0 1 1 1 1	1 0 1 0 1
16	1 0 0 0 0	1 0 1 1 0
17	1 0 0 0 1	1 0 1 1 1
18	1 0 0 1 0	1 1 0 0 0
19	1 0 0 1 1	1 1 0 0 1

$$C = K + Z_8 Z_4 + Z_8 Z_2$$

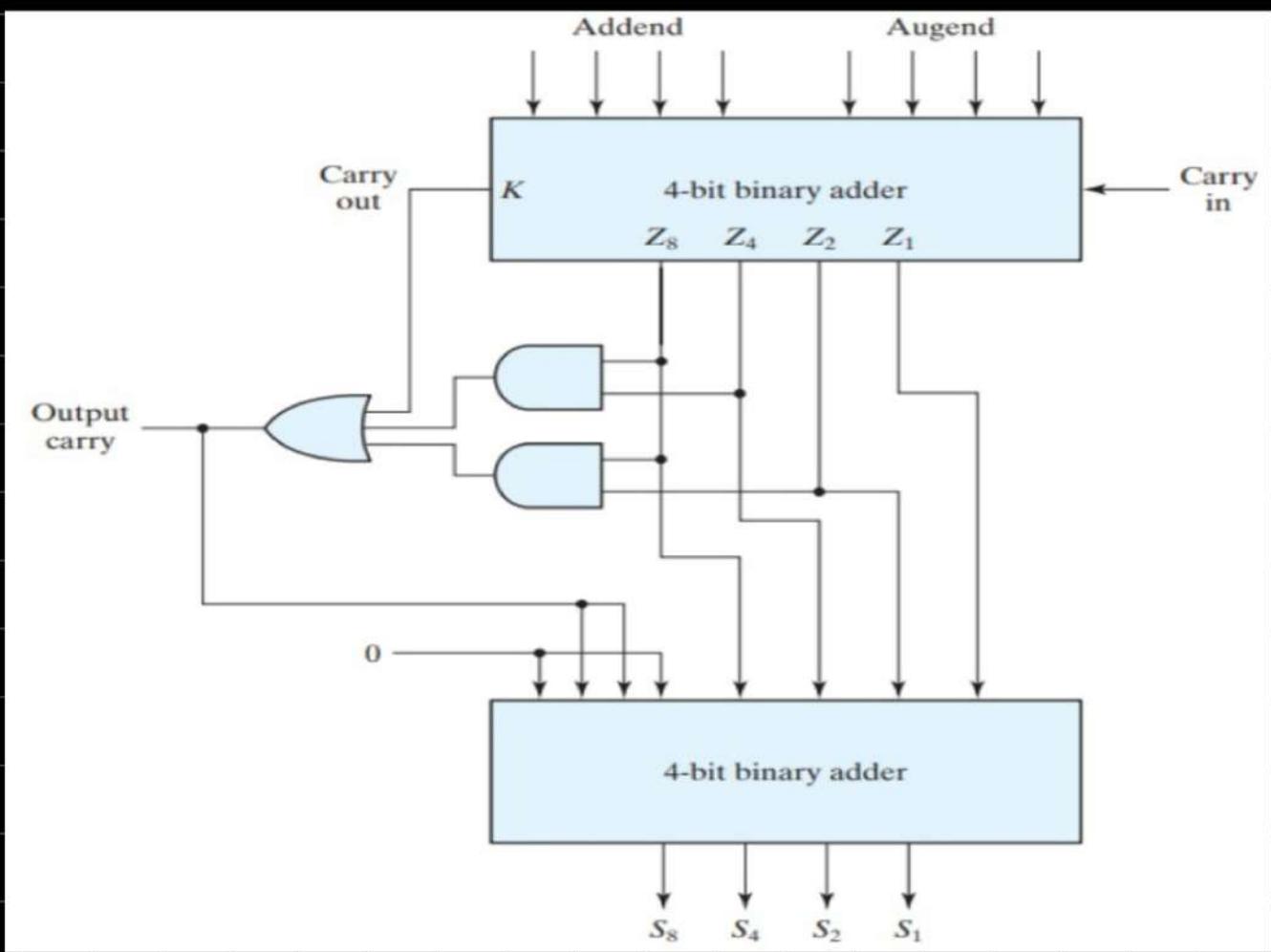

$$\begin{array}{r}
 789 + 123 \Rightarrow \\
 \begin{array}{r}
 1 \quad | \quad 1 \quad | \quad 1 \quad | \quad 0 \quad 0 \quad 0 \quad 0 \quad | \quad 1 \quad 0 \quad 0 \quad 1 \\
 0 \quad 1 \quad | \quad 1 \quad | \quad 0 \quad 0 \quad 1 \quad 0 \quad | \quad 1 \quad 0 \quad 1 \quad 1 \\
 0 \quad 0 \quad 0 \quad 1 \quad | \quad 0 \quad 0 \quad 1 \quad 0 \quad | \quad 0 \quad 0 \quad 1 \quad 1 \\
 \hline
 1 \quad 0 \quad 0 \quad 1 \quad | \quad 1 \quad 0 \quad 1 \quad 1 \quad | \quad 1 \quad 1 \quad 0 \quad 0 \\
 \hline
 0 \quad 1 \quad 1 \quad 0 \quad | \quad 0 \quad 0 \quad 1 \quad 0 \quad | \quad 1 \quad 1 \quad 1 \quad 0 \\
 \hline
 0 \quad 0 \quad 0 \quad 1 \quad | \quad 1 \quad 1 \quad 1 \quad 0 \quad | \quad 1 \quad 1 \quad 1 \quad 0 \\
 \end{array}
 \end{array}$$

9 1 2

BINARY MULTIPLIERS

each multiplication \rightarrow partial product
 sum of partial products \rightarrow final product

J -bit \times K -bit

$J \times K$ AND gates

$(J-1)K$ bits adders

$(J+K)$ bits products




1010×1011

$$\begin{array}{r}
 & 1 & 0 & 1 & 0 \\
 \times & 1 & 0 & 1 & 1 \\
 \hline
 & 1 & 0 & 1 & 0 \\
 , & 1 & 0 & 1 & 0 \\
 0 & 0 & 0 & 0 \\
 \hline
 1 & 0 & 1 & 0 \\
 \hline
 1 & 1 & 0 & 1 & 1 & 1 & 0
 \end{array}$$

→ partial product 1
 → partial product 2
 → partial product 3
 → partial product 4

2 bit \times 2 bit:
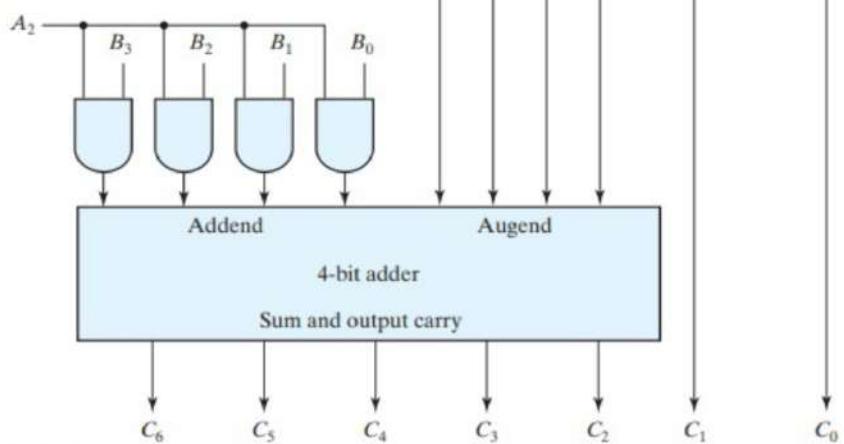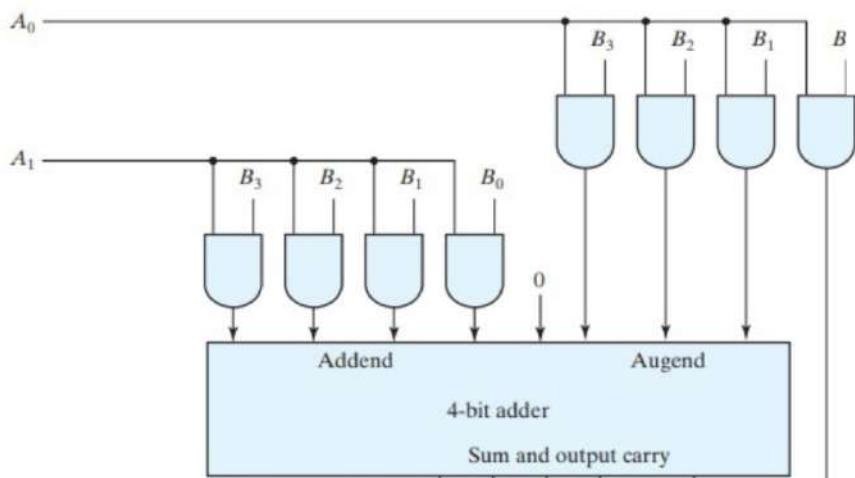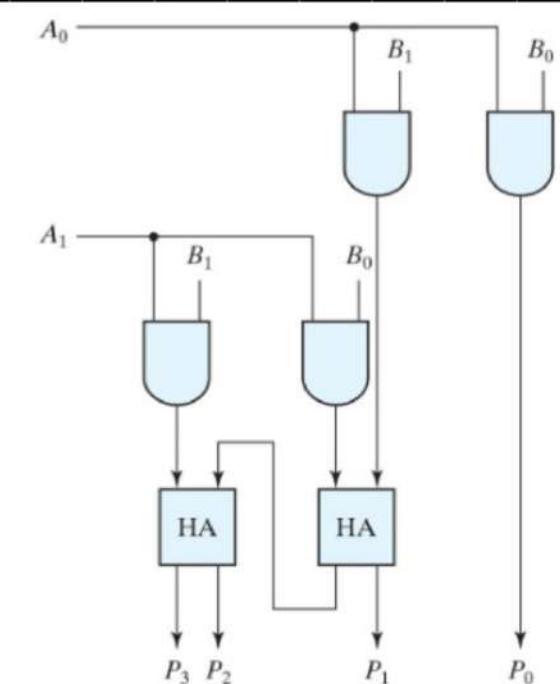
$$\begin{array}{r}
 B_1 \quad B_0 \\
 A_1 \quad A_0 \\
 \hline
 A_0B_1 \quad A_0B_0 \\
 \hline
 A_1B_1 \quad A_1B_0 \\
 \hline
 P_3 \quad P_2 \quad P_1 \quad P_0
 \end{array}$$



4 bit by 3 bit

J = 4

K = 3

product \rightarrow 7 bit
 address \rightarrow 2 4-bit
 and gate \rightarrow 12

MAGNITUDE COMPARATORS

Combinational circuit that compares two numbers A & B and determine their relative magnitude

$$A > B, A = B, A < B$$

Equality of each pair of bits can be expressed with XNOR

$$x_i = A_i B_i + A_i' B_i' \quad i=0,1,2,3$$

1 BIT COMPARATOR

A	B	$A = B$	$A > B$	$A < B$
0	0	1	0	0
0	1	0	0	1
1	0	0	1	0
1	1	1	0	0

$$\text{output} = \overline{A} \overline{B} + AB$$

1 hot encoding
→ 1 high

n-bit comparator


$2n$ variables

2^{2n} rows

$$A > B = A \overline{B}$$

$$A = B = A \odot B$$

$$A < B = \overline{A} B$$

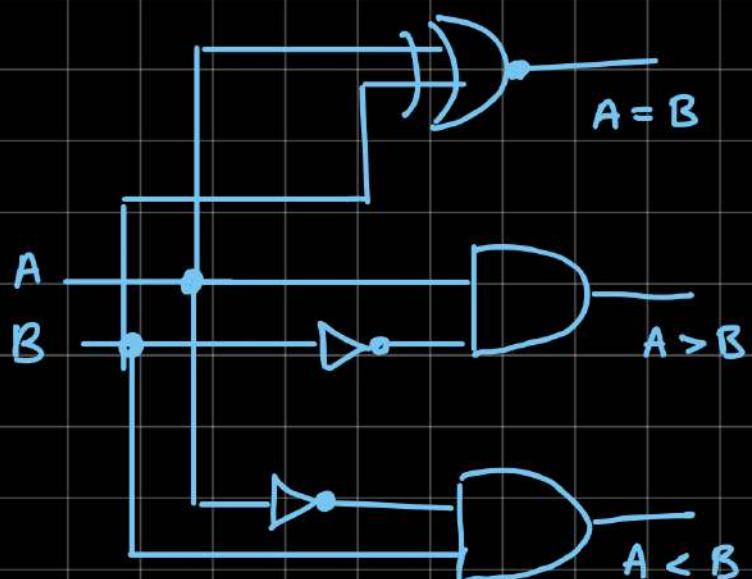

2 BIT COMPARATOR


A_1	A_0	B_1	B_0	$A > B$	$A = B$	$A < B$
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

using K-Maps, we get,

$$A > B = A_1 \bar{B}_1 + A_0 \bar{B}_1 \bar{B}_0 + A_0 A_1 \bar{B}_0 \\ = A_1 \bar{B}_1 + (A_1 \oplus B_1) A_0 \bar{B}_0$$

$$A = B = (A_1 \oplus B_1) (A_0 \oplus B_0)$$
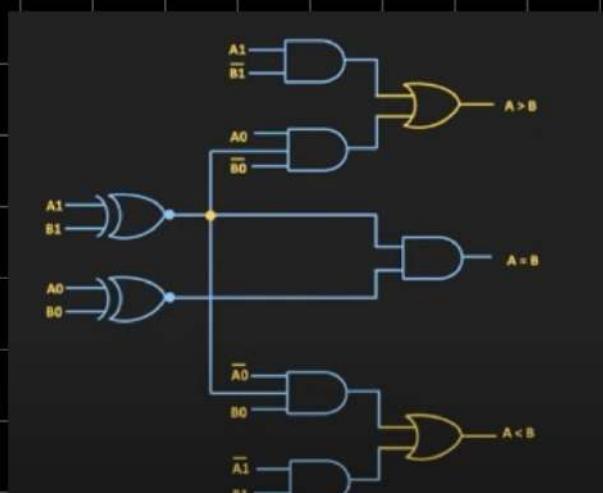
$$A < B = \bar{A}_1 B_1 + B_0 \bar{A}_1 \bar{A}_2 + \bar{A}_0 B_0 B_1 \\ = \bar{A}_1 B_1 + (A_1 \oplus B_1) \bar{A}_0 B_0$$



(A pattern can be noticed with the equations if looked at carefully)


4 BIT COMPARATOR

$$A = A_3 A_2 A_1 A_0 \quad \& \quad B = B_3 B_2 B_1 B_0$$

$$A = B = (A_3 \odot B_3) (A_2 \odot B_2) (A_1 \odot B_1) \\ \cdot (A_0 \odot B_0)$$

- If
- (1) $A_3 > B_3 \quad A > B = A_3 \overline{B_3} + (A_3 \odot B_3) A_2 \overline{B_2}$
 - (2) $A_3 = B_3 \quad \& \quad A_2 > B_2 \quad + (A_3 \odot B_3) (A_2 \odot B_2) A_1 \overline{B_1}$
 - (3) $A_3 = B_3 \quad \& \quad A_2 = B_2, A_1 > B_1 \quad + (A_3 \odot B_3) (A_2 \odot B_2) (A_1 \odot B_1) A_0 \overline{B_0}$
 - (4) $A_3 = B_3 \quad \& \quad A_2 = B_2, A_1 = B_1$
then $A_0 > B_0$

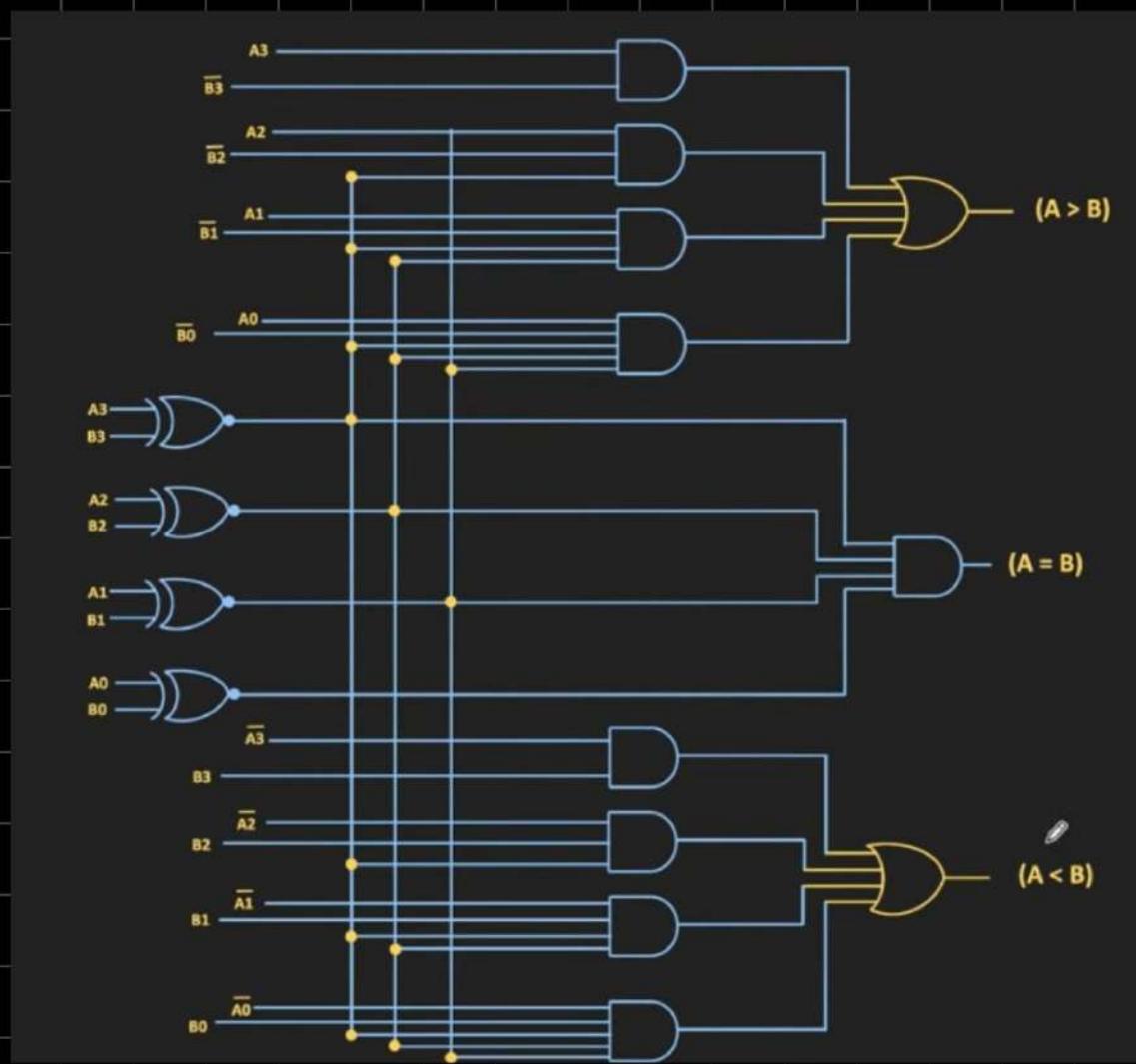
$$A < B = \overline{A_3} B_3 + (A_3 \odot B_3) \overline{A_2} B_2 \\ + (A_3 \odot B_3) (A_2 \odot B_2) \overline{A_1} B_1 \\ + (A_3 \odot B_3) (A_2 \odot B_2) (A_1 \odot B_1) \overline{A_0} B_0$$



DECODERS



1 : 2 Decoder

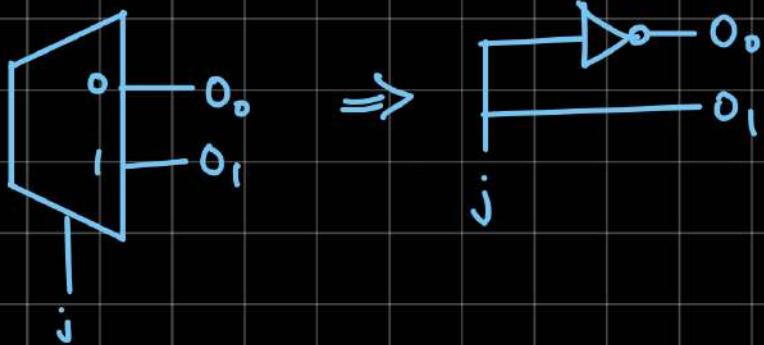

j	O ₀	O ₁
0	1	0
1	0	1

$$O_0 = j'$$

$$O_1 = j$$

2 : 4 Decoder

x	y	F ₀	F ₁	F ₂	F ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1



(Fill 1 diagonally)

$$F_0 = x'y'$$

$$F_1 = x'y$$


$$F_2 = xy'$$

$$F_3 = xy$$

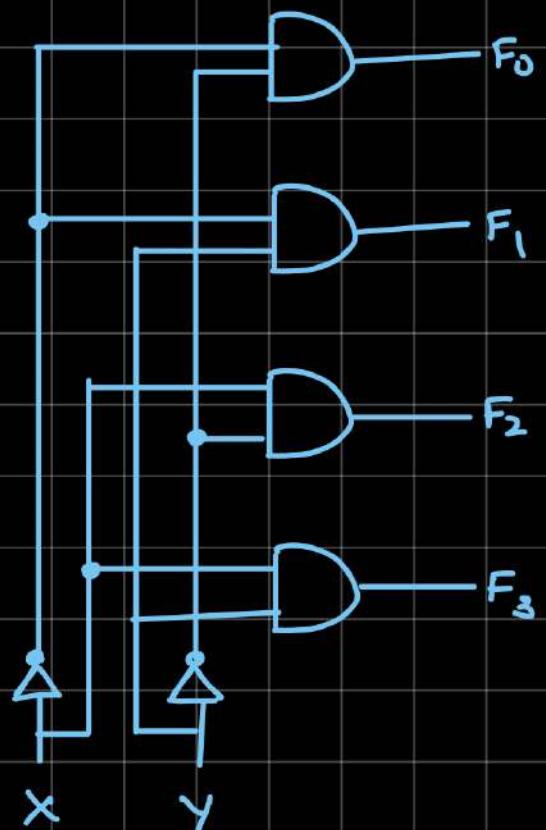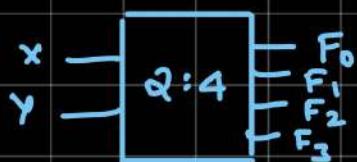

3:8 DECODER

X	Y	Z	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

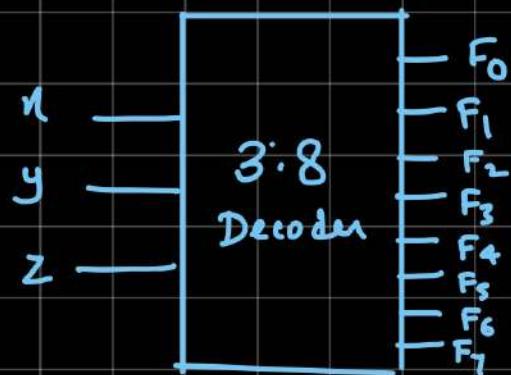

$$F_0 = x'y'z'$$

$$F_1 = x'y'z$$

$$F_2 = x'yz'$$


$$F_3 = x'yz$$

$$F_4 = xy'z'$$

$$F_5 = xy'z$$

$$F_6 = xyz'$$

$$F_7 = xyz$$

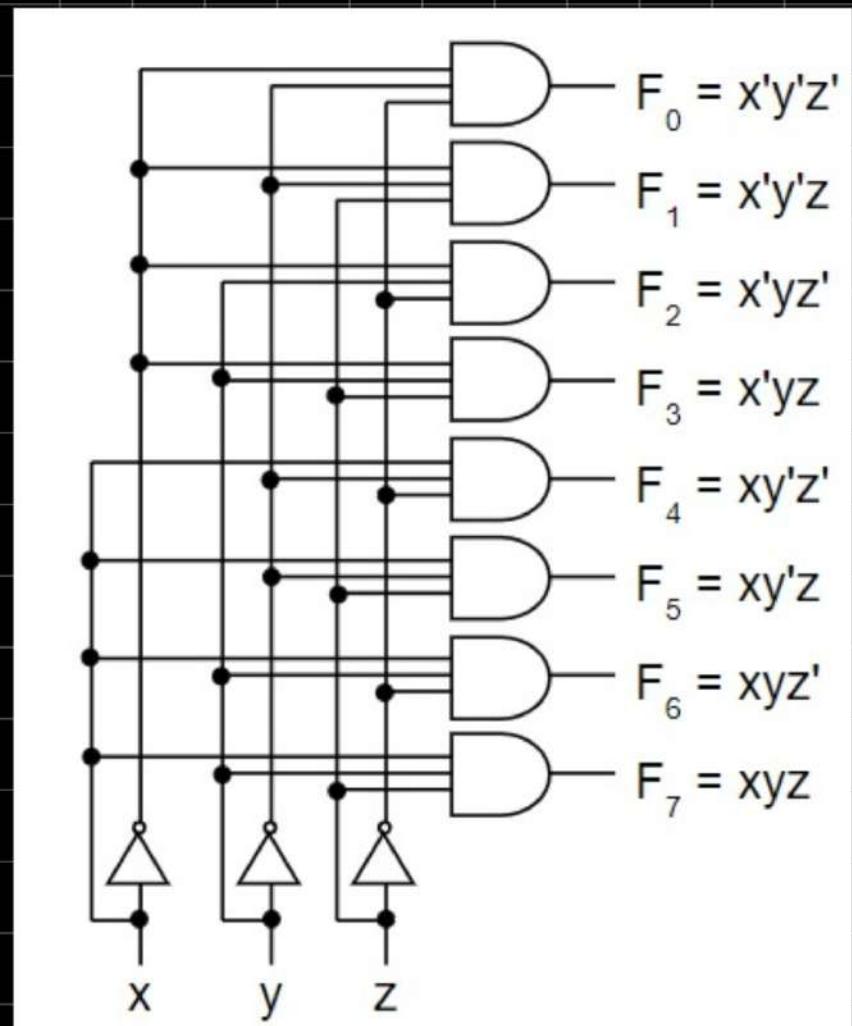


DECODERS WITH NAND GATES

with enable

\Rightarrow use of NANDs only
when $E=0$

E	A	B	D ₀	D ₁	D ₂	D ₃
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

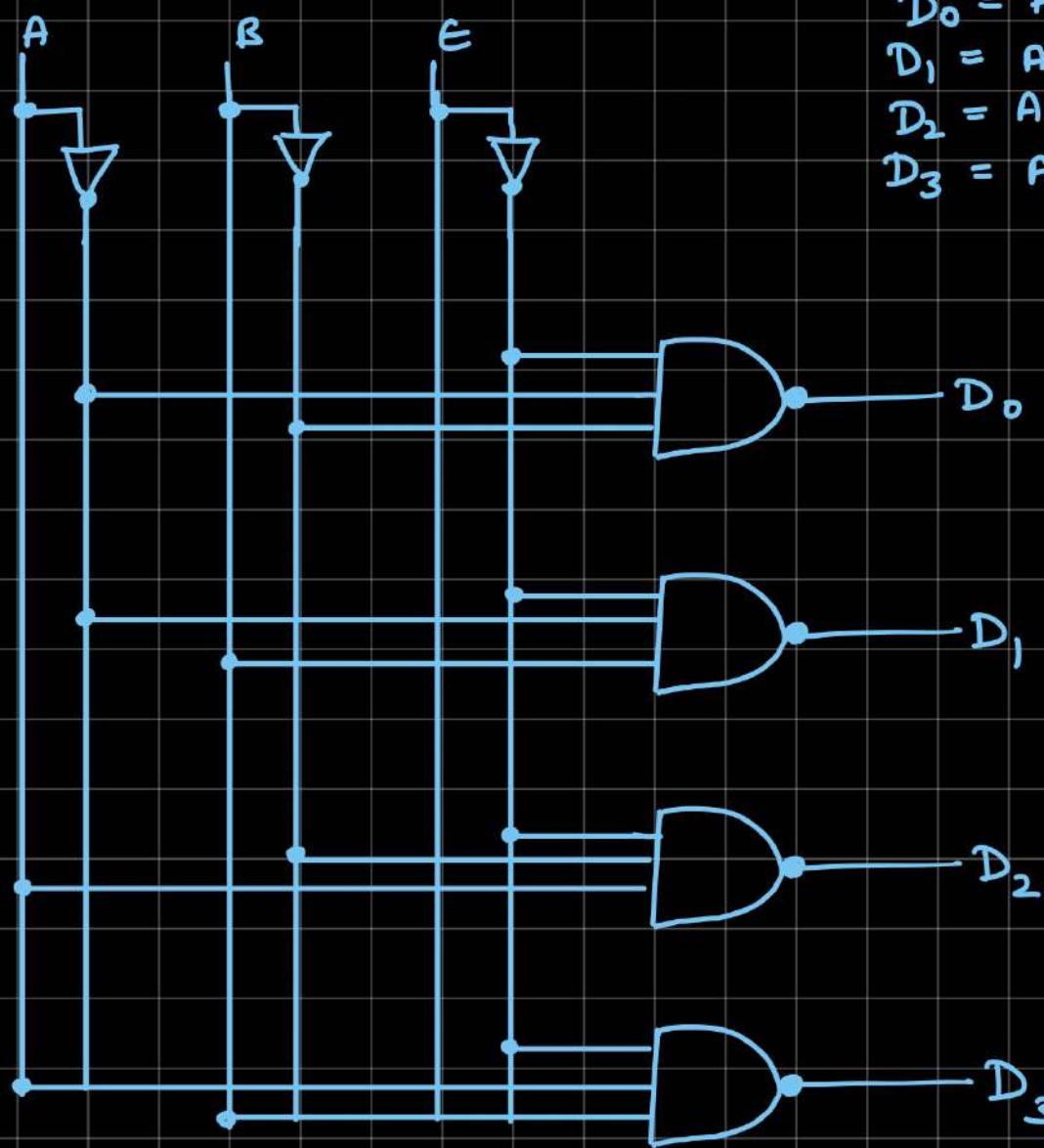


$$D_0 = A'B'E'$$

$$D_1 = A'B'E'$$


$$D_2 = AB'E'$$

$$D_3 = ABE'$$

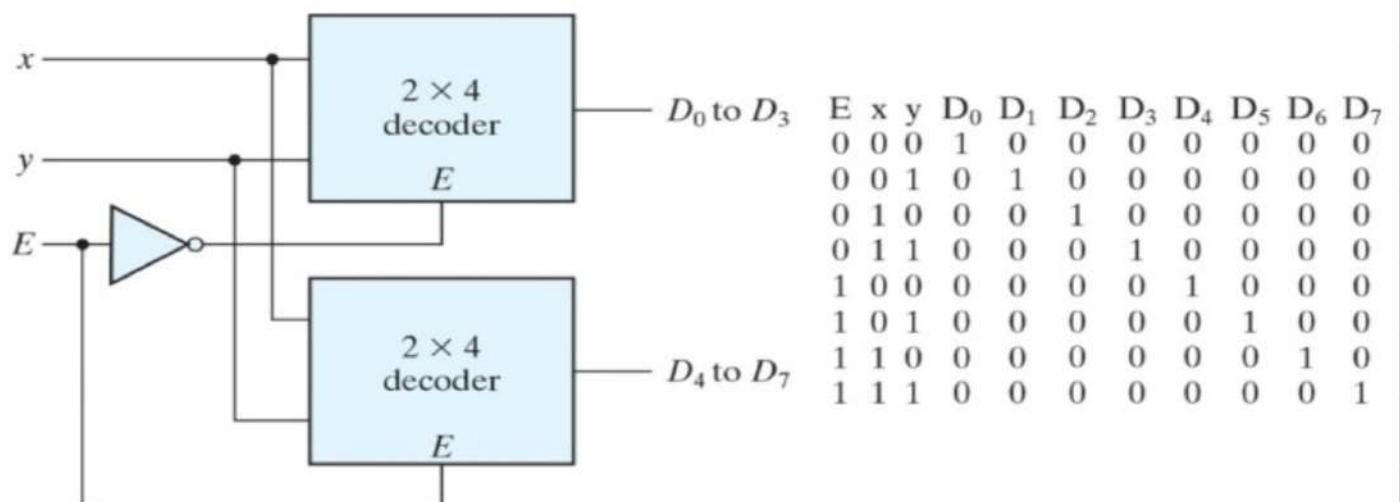3 x 8 decoder constructed with two 2 x 4 decoders.



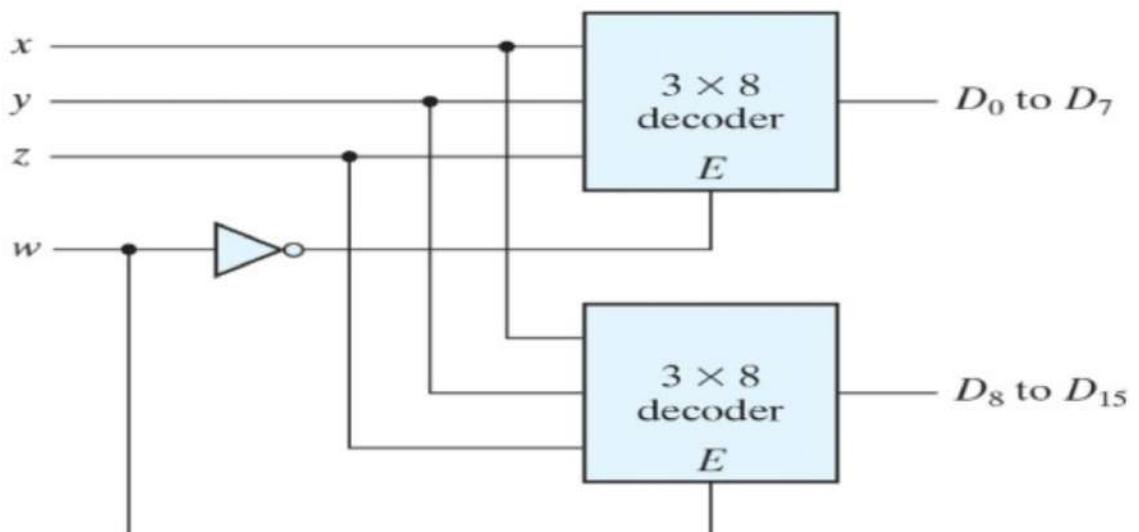4 x 16 decoder constructed with two 3 x 8 decoders.



Enable can also be active high

In this example, only one decoder can be active at a time.


x, y, z effectively select output line for w

Implementation of full adder with a 3:8 decoder

x	y	z	s	c	
0	0	0	0	0	$\rightarrow F_0$
0	0	1	1	0	$\rightarrow F_1$
0	1	0	1	0	$\rightarrow F_2$
0	1	1	0	1	$\rightarrow F_3$
1	0	0	1	0	$\rightarrow F_4$
1	0	1	0	1	$\rightarrow F_5$
1	1	0	0	1	$\rightarrow F_6$
1	1	1	1	1	$\rightarrow F_7$

$$S = \sum(1, 2, 4, 7)$$


$$C = \sum(3, 5, 6, 7)$$

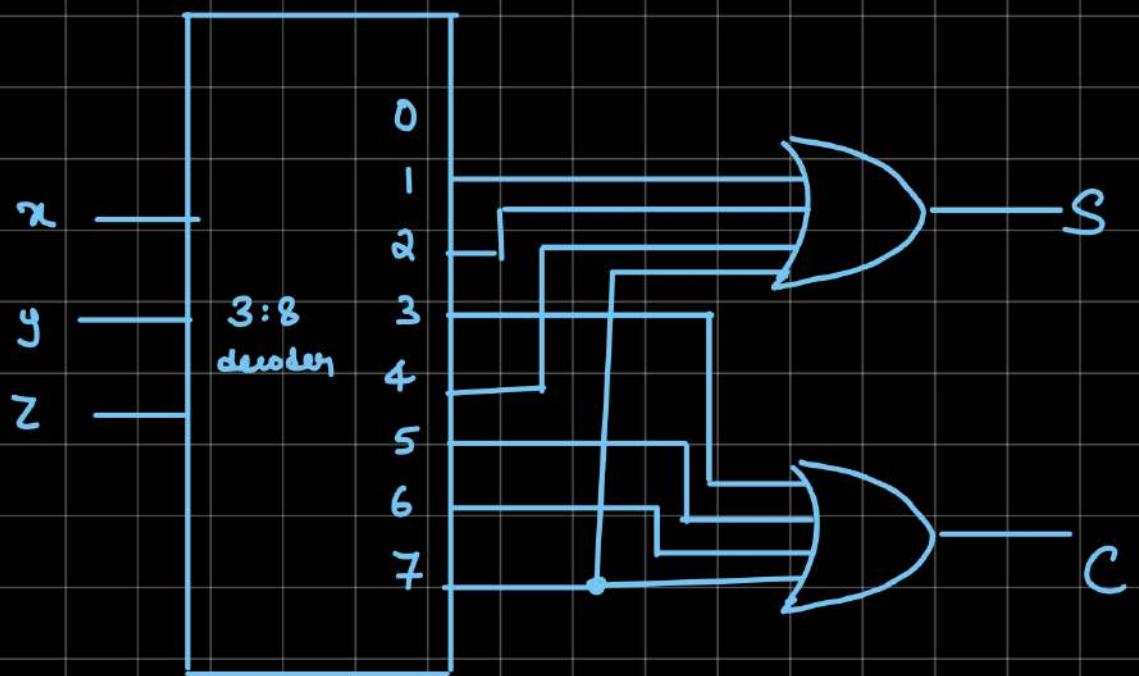


Build XNOR gate using 2:4 decoder

x	y	$x \odot y$	
0	0	1	$\rightarrow F_0$
0	1	0	$\rightarrow F_1$
1	0	0	$\rightarrow F_2$
1	1	1	$\rightarrow F_3$

$$F = \sum(0, 3)$$

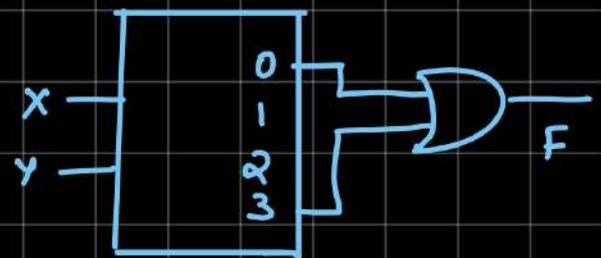

ENCODERS

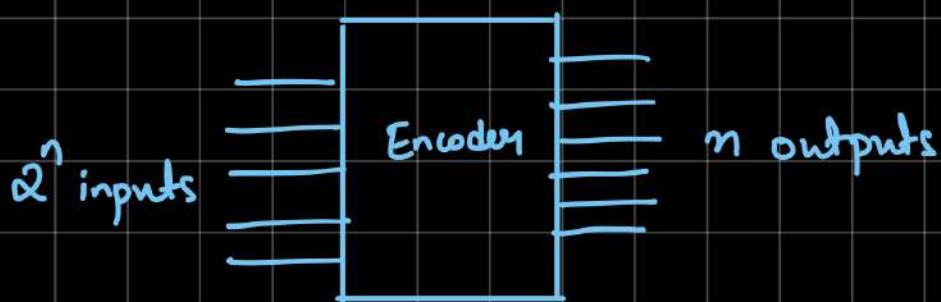


4:2 ENCODER


input				output	
y_0	y_1	y_2	y_3	A	B
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

$$A = y_3 + y_2$$

$$B = y_3 + y_1$$

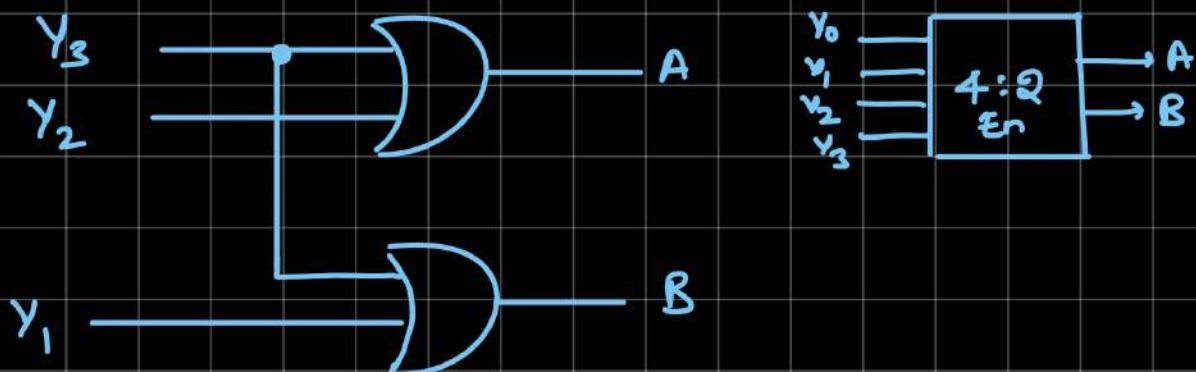

8:3
Encoder

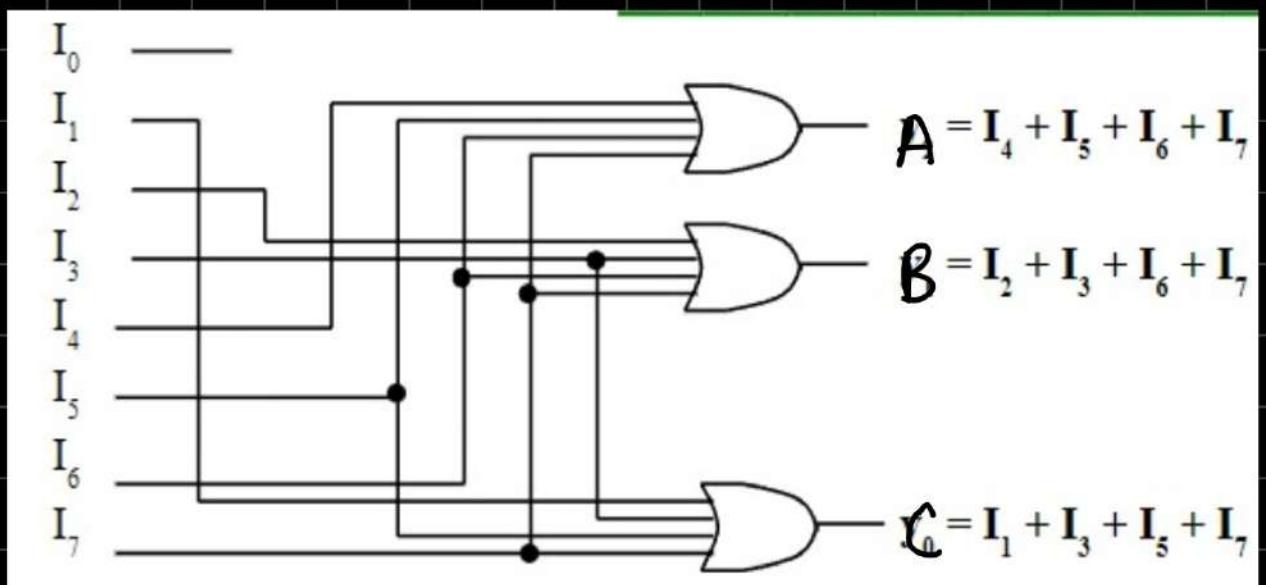

8 : 3 ENCODER

I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7	A	B	C
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

$$A = I_4 + I_5 + I_6 + I_7$$

$$B = I_2 + I_3 + I_6 + I_7$$

$$C = I_1 + I_3 + I_5 + I_7$$

PRIORITY ENCODERS

- encoder circuit that includes a priority function
- if 2 or more inputs are equal to 1 at the same time
then input having higher priority will take precedence
- valid bit indicator → set to 1 if one or more
input is 1
if $V=0$, the don't care for output

4 : 2

Inputs				Outputs		
D_0	D_1	D_2	D_3	x	y	v
0	0	0	0	x	x	0
1	0	0	0	0	0	1
x	1	0	0	0	1	1
x	x	1	0	1	0	1
x	x	x	1	1	1	1

For x :

$D_3 D_2$	00	01	11	10
$D_1 D_0$	00	X	1 1 1 1	1 1 1 1
01	1 1 1 1	X	1 1 1 1	1 1 1 1
11	1 1 1 1	1 1 1 1	X	1 1 1 1
10	1 1 1 1	1 1 1 1	1 1 1 1	X


For y :

$D_3 D_2$	00	01	11	10
$D_1 D_0$	00	X	1 1 1 1	1 1 1 1
01	1 1 1 1	1 1 1 1	X	1 1 1 1
11	1 1 1 1	1 1 1 1	1 1 1 1	X
10	1 1 1 1	1 1 1 1	1 1 1 1	1 1 1 1

$$x = D_3 + D_2$$

$$y = D_1 D_2' + D_3$$

$$V = D_0 + D_1 + D_2 + D_3$$

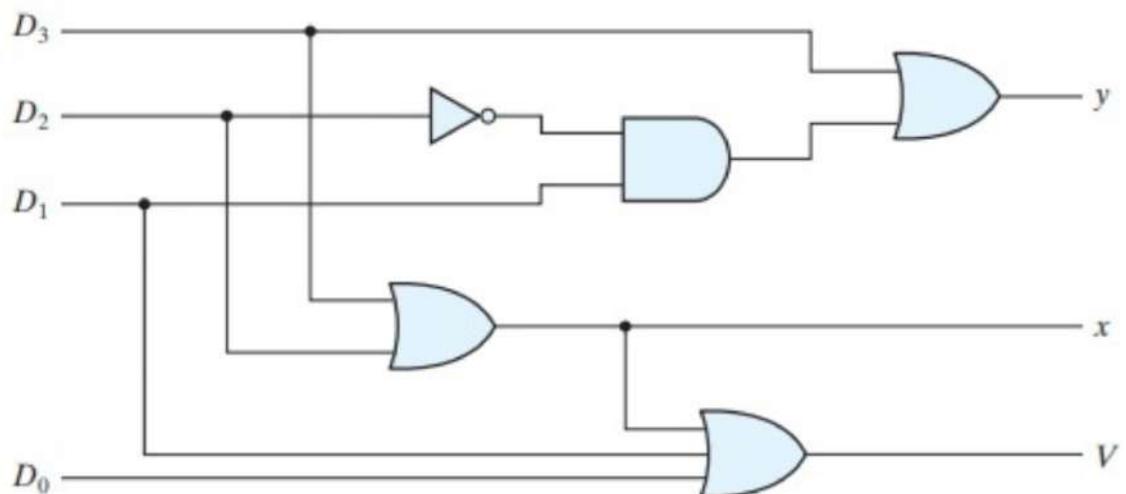

8 : 3 ENCODER

Inputs								Outputs			
I ₀	I ₁	I ₂	I ₃	I ₄	I ₅	I ₆	I ₇	y ₂	y ₁	y ₀	Idle
0	0	0	0	0	0	0	0	X	X	X	1
1	0	0	0	0	0	0	0	0	0	0	0
X	1	0	0	0	0	0	0	0	0	1	0
X	X	1	0	0	0	0	0	0	1	0	0
X	X	X	1	0	0	0	0	0	1	1	0
X	X	X	X	1	0	0	0	1	0	0	0
X	X	X	X	X	1	0	0	1	0	1	0
X	X	X	X	X	X	1	1	1	1	1	0


Priority Encoder :

$H_7 = I_7$ (Highest Priority)
 $H_6 = I_{16} \cdot I_7'$
 $H_5 = I_{15} \cdot I_6 \cdot I_7'$
 $H_4 = I_{14} \cdot I_5' \cdot I_6 \cdot I_7'$
 $H_3 = I_{13} \cdot I_4' \cdot I_5' \cdot I_6 \cdot I_7'$
 $H_2 = I_{12} \cdot I_3' \cdot I_4' \cdot I_5' \cdot I_6 \cdot I_7'$
 $H_1 = I_{11} \cdot I_2' \cdot I_3' \cdot I_4' \cdot I_5' \cdot I_6 \cdot I_7'$
 $H_0 = I_{10} \cdot I_1' \cdot I_2' \cdot I_3' \cdot I_4' \cdot I_5' \cdot I_6 \cdot I_7'$
 $IDLE = I_0' \cdot I_1' \cdot I_2' \cdot I_3' \cdot I_4' \cdot I_5' \cdot I_6' \cdot I_7'$

Encoder


$$Y_0 = I_1 + I_3 + I_5 + I_7$$

$$Y_1 = I_2 + I_3 + I_6 + I_7$$
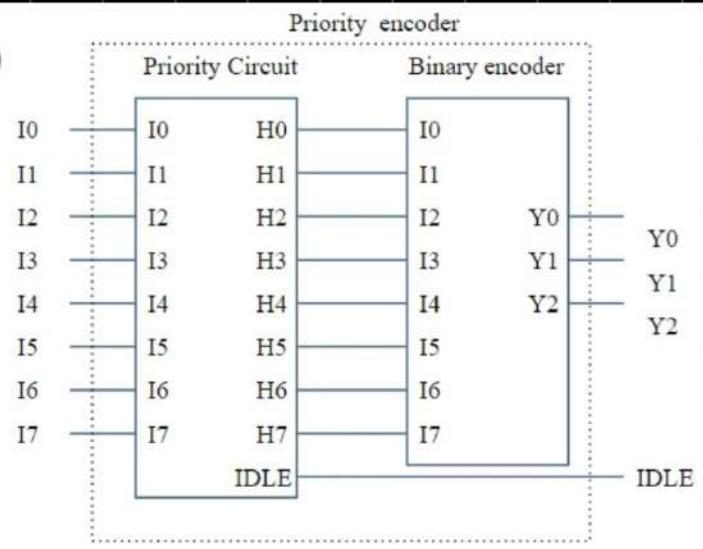
$$Y_2 = I_4 + I_5 + I_6 + I_7$$


ENCODER APPLICATION

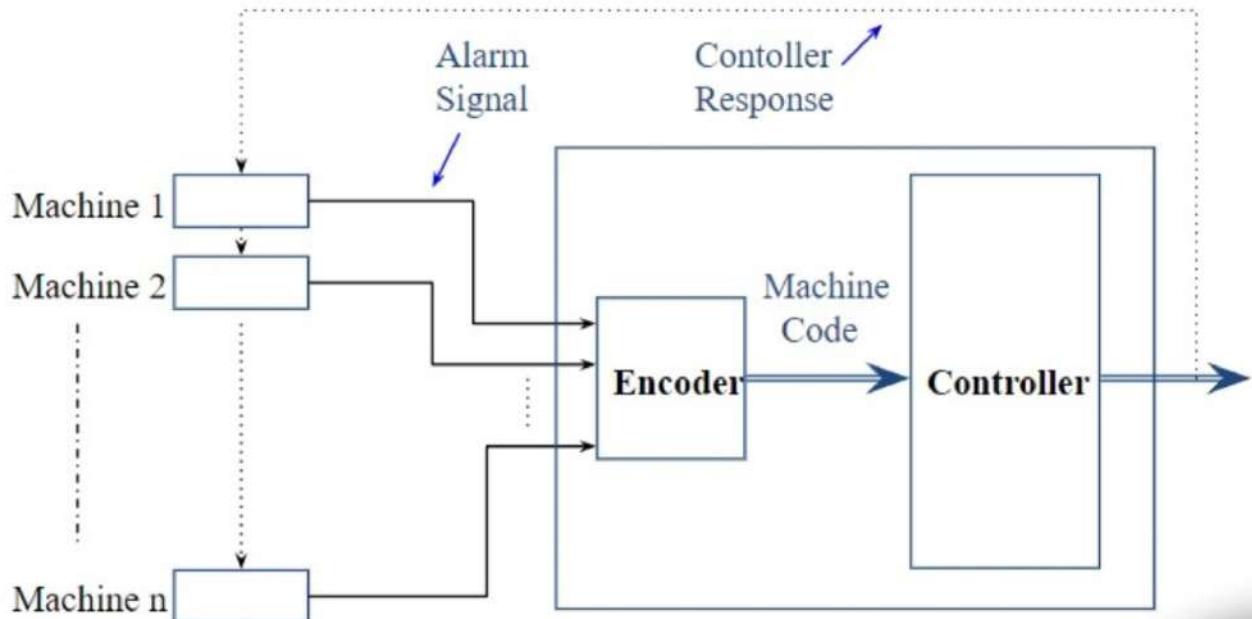- encoder identifies the requester & encodes the value
- controller accepts digital inputs



MACHINES → different machines connected to the encoder

ENCODER → primary role to identify which machine is sending request & then encoding the value to machine code
also generates alarm signal if needed

CONTROLLER → Receives the encoded machine code from encoder

Based on the machine code, controller performs specific actions such as sending signals back to machine

ALARM SIGNAL → An alert generated by encoder if certain condition is met

→ Malfunction / Process completion / any other situation that needs immediate action

CONTROLLER RESPONSE →

A response sent back to the machine or trigger other actions that are needed

APPLICATION


Encoder → computer (keyboard)

Priority encoder → microprocessor

Decoders → memory systems

MULTIPLEXER // MUX

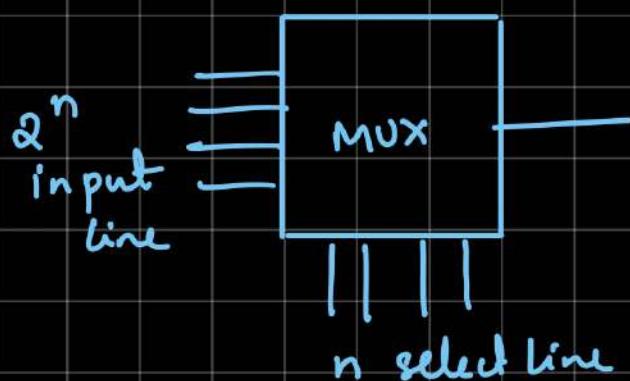$n:1$ MUX → 2^n input
n select lines
1 output





2:1 MUX


S	A	B	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

when $S=0, Y=A$

$S=1, Y=B$

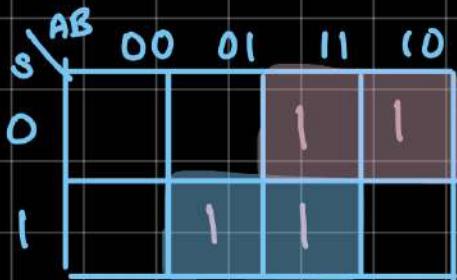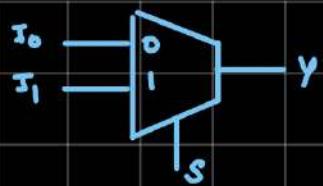


$$Y = S'A + SB$$

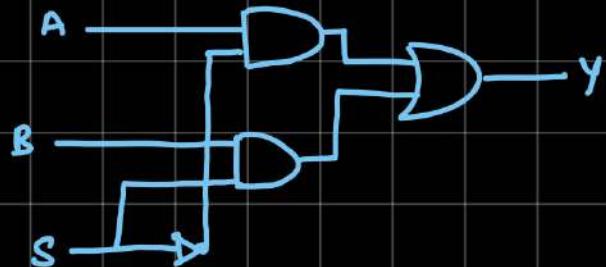


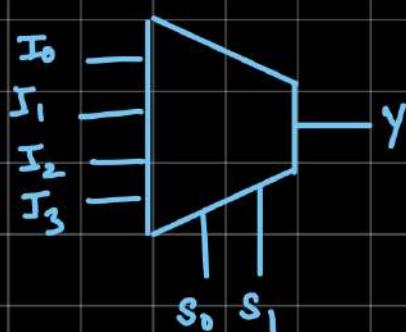4:1 MUX

Implement a 4:1 MUX, realise the circuit & TT by considering the select lines




S ₀	S ₁	Y
0	0	I ₀
0	1	I ₁
1	0	I ₂
1	1	I ₃

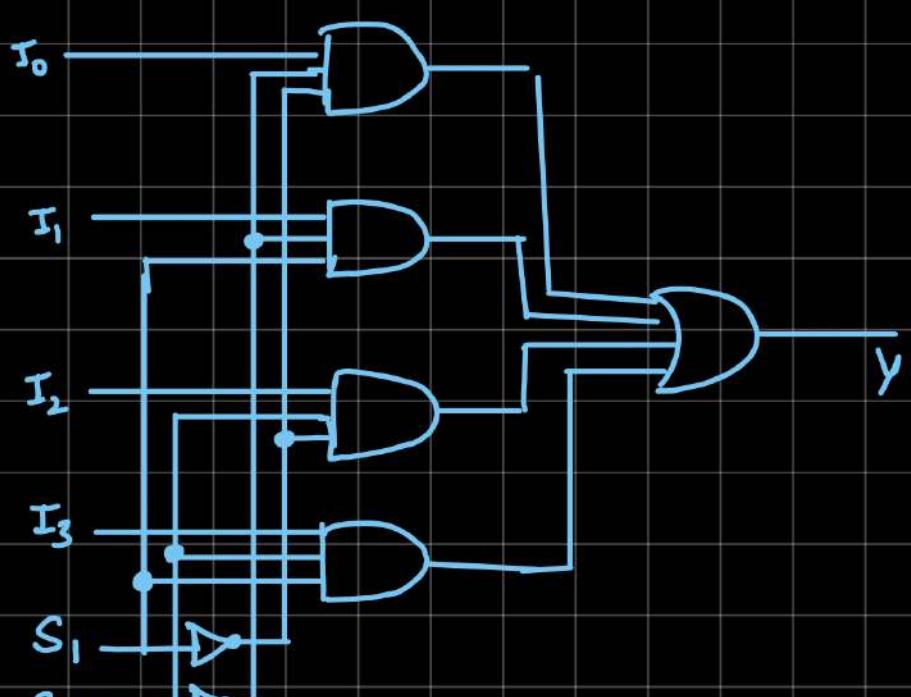

$$Y = \bar{S}_0 \bar{S}_1 I_0 + \bar{S}_0 S_1 I_1 + S_0 \bar{S}_1 I_2 + S_0 S_1 I_3$$


Implement 4:1 MUX using 2:1 MUX

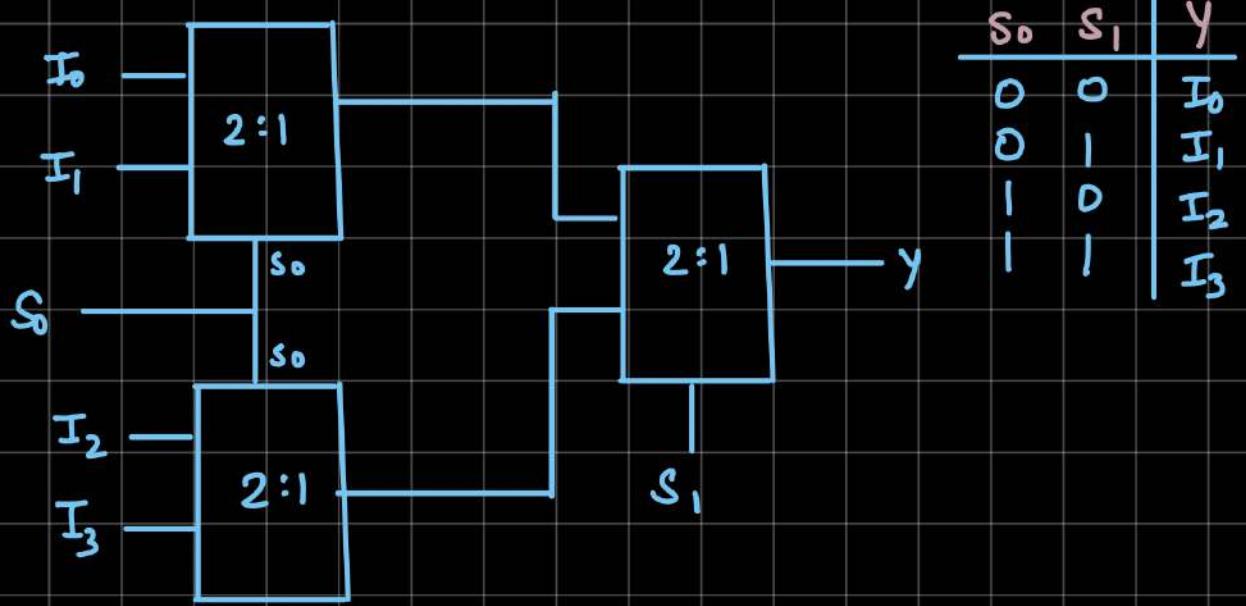

Design an XOR gate using 2:1 MUX

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

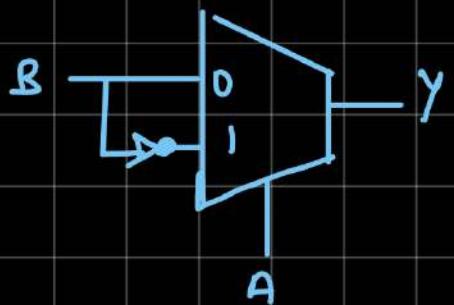Let A be selected line
when $A=0, Y=B$
 $A=1, Y=\bar{B}$



Implement the boolean function $F = \Sigma(1, 2, 6, 7)$ using a MUX

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

When

$A=0, B=0$

$Y=C$

$A=0, B=1$

$y=\bar{C}$


$A=1, B=0$

$Y=0$

$A=1, B=1$

$Y=1$

* follow the
order when
drawing MUX

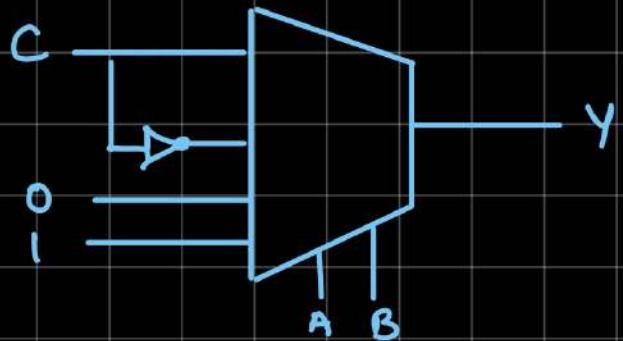


Using 4:1 MUX design the following function

$$Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$$

$$\begin{aligned} Y &= A\bar{B}C + A\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}BC \\ &= \Sigma(0, 3, 4, 5) \end{aligned}$$

A	B	C	Y	when
0	0	0	1	$A=0, B=0$
0	0	1	0	$Y = \bar{C}$
0	1	0	0	$A=0, B=1$
0	1	1	1	$Y = C$
1	0	0	1	$A=1, B=0$
1	0	1	1	$Y = 1$
1	1	0	0	$A=1, B=1$
1	1	1	0	$Y = 0$

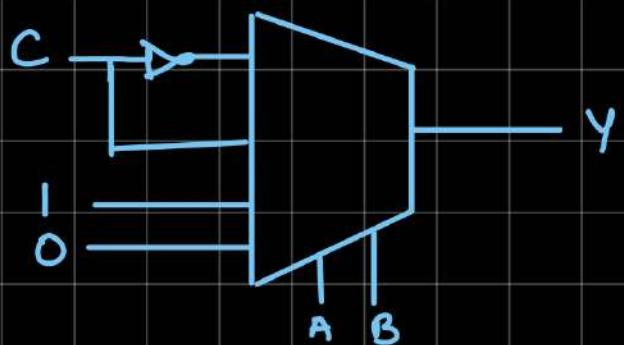

Implement the boolean fn $F(A, B, C, D) = \Sigma(1, 3, 4, 11, 12, 13, 14, 15)$
using a 8:1 MUX

A	B	C	D	Y	when
0	0	0	0	0	$A=0, B=0, C=0$ $Y=D$
0	0	0	1	1	$A=0, B=0, C=1$ $Y=D$
0	0	1	0	0	$A=0, B=1, C=0$ $Y=\bar{D}$
0	0	1	1	1	$A=0, B=1, C=1$ $Y=0$
0	1	0	0	1	$A=1, B=0, C=0$ $Y=0$
0	1	0	1	0	$A=1, B=0, C=1$ $Y=D$
0	1	1	0	0	$A=1, B=1, C=0$ $Y=1$
0	1	1	1	1	$A=1, B=1, C=1$ $Y=1$
1	0	0	0	0	
1	0	0	1	0	
1	0	1	0	0	
1	0	1	1	1	
1	1	0	0	1	
1	1	0	1	1	
1	1	1	0	1	
1	1	1	1	1	

